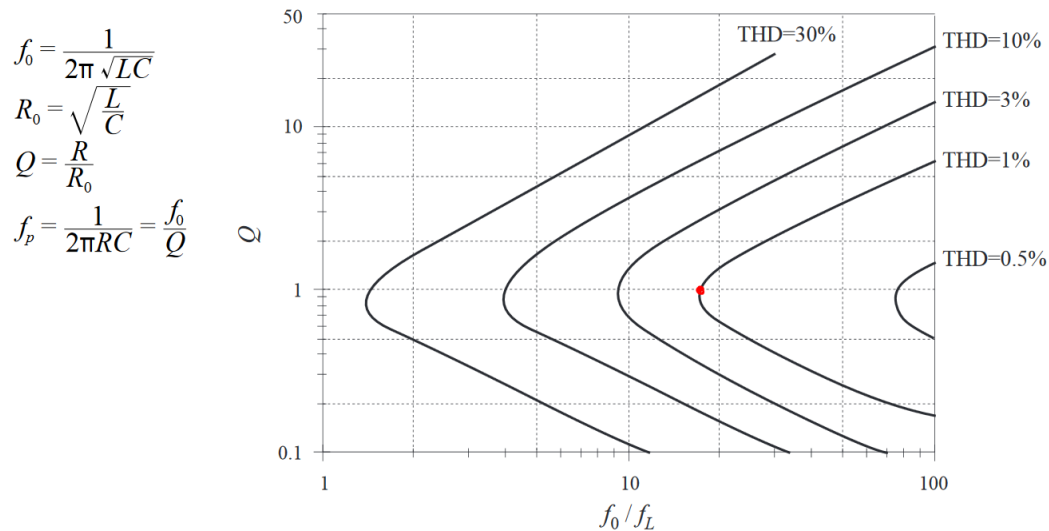


Homework 11 Solutions:

Using the Curve shown below:

Approximate THD




We can use the THD=1% contour curve to design our filter. The problem states that you want to minimize the corner frequency f_0 and still maintain low Q . Minimizing the corner frequency will provide the most attenuation from the filter at switching frequencies of potential downstream switching converters. While you can select to have a very little Q , the resulting f_0 will not be minimized. So the red dot indicates the point at which you minimize the filter corner frequency f_0 and the filter Q . From the curve:



2 $Q = 1$


1 $\frac{f_0}{f_L} = 18 \rightarrow f_0 = 18 * 50 = 900\text{Hz}$

2 $C = \frac{Q}{2\pi R f_0} = \frac{1}{2\pi * 40 * 900} = 4.42\mu\text{F}$

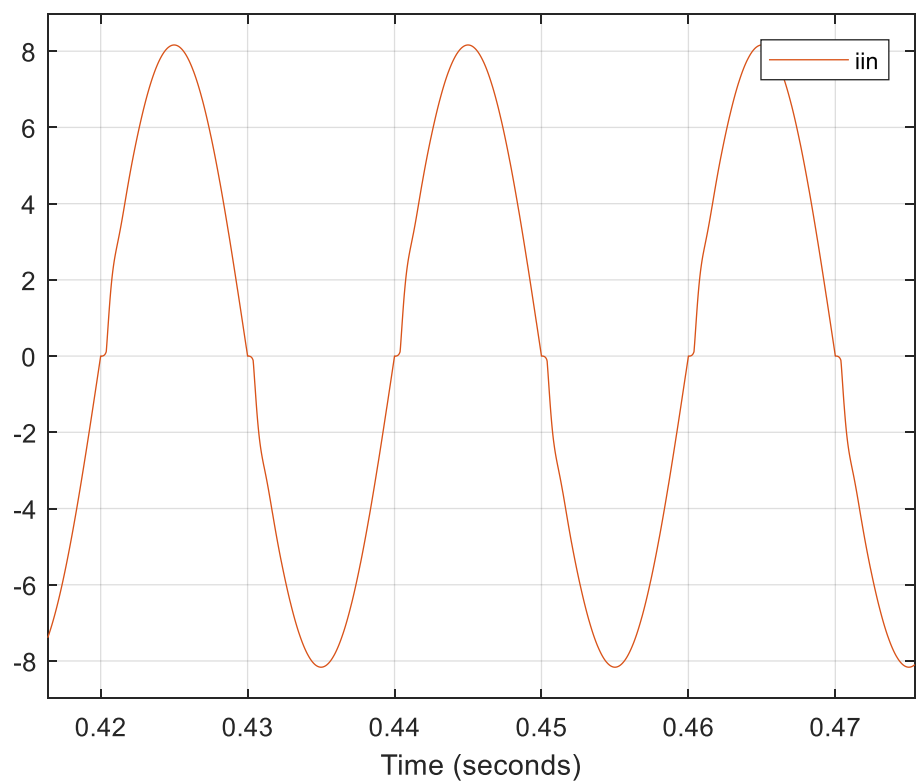2 $L = \frac{1}{4\pi^2 C f_0^2} = 7.07\text{mH}$



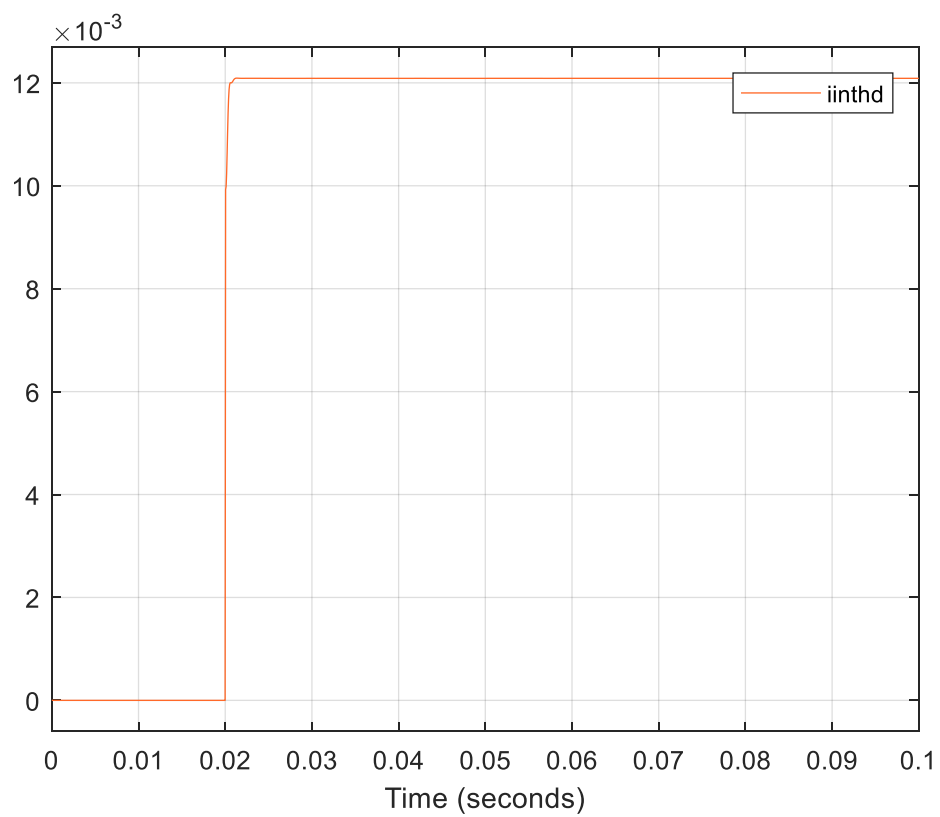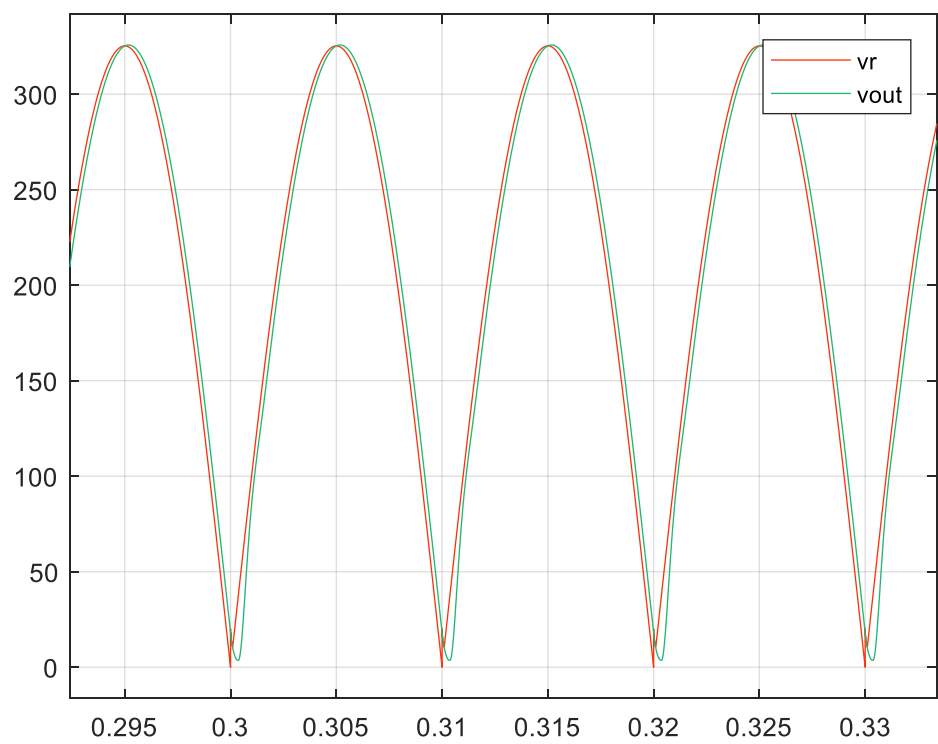

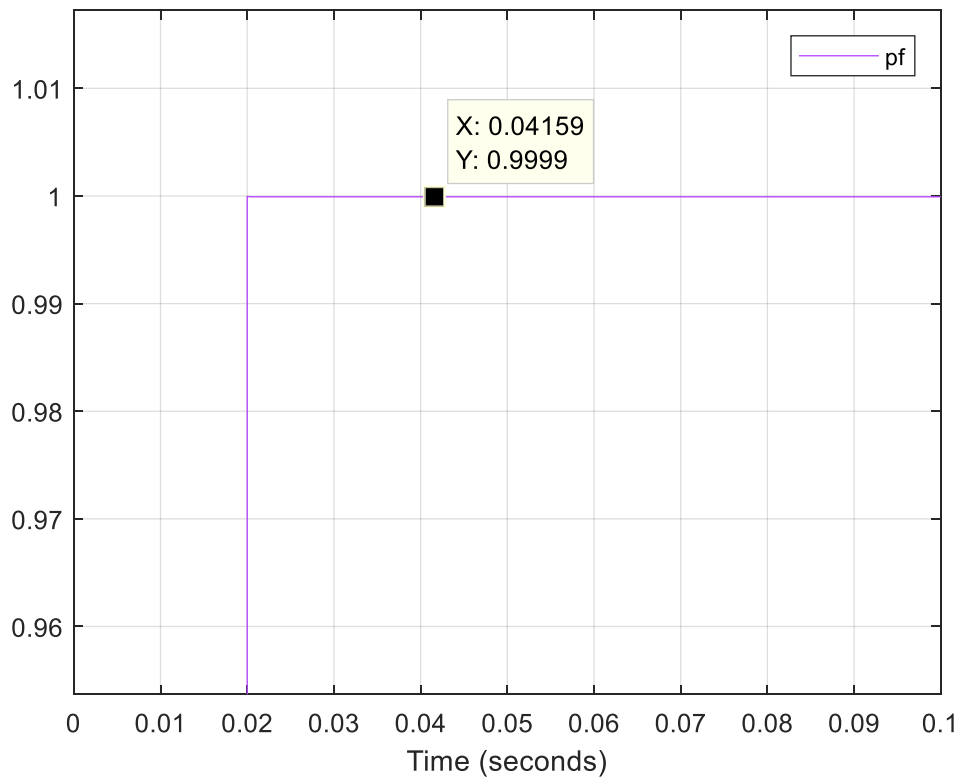

Given that the voltage output voltage has a very large variation due to the rectified sine wave, we would need a converter that can regulate an output voltage over this entire range including zero. A boost, buck-boost or flyback all have voltage transfer ratios, $M(d)$, that can achieve infinity (i.e. $v_{in}=0$)