



Johns Hopkins Engineering

Power Electronics 525.725

Module 2 Lecture 2a
Boost Converter Simulink Simulation



Boost Converter

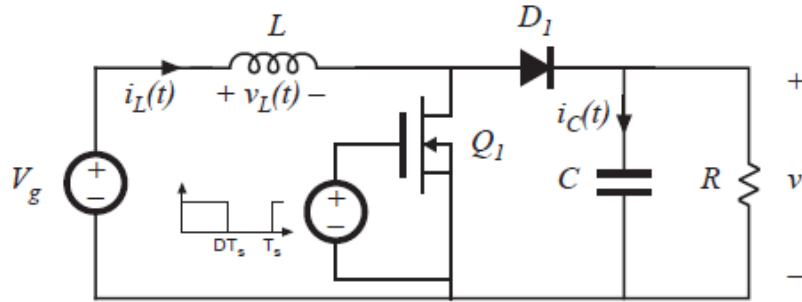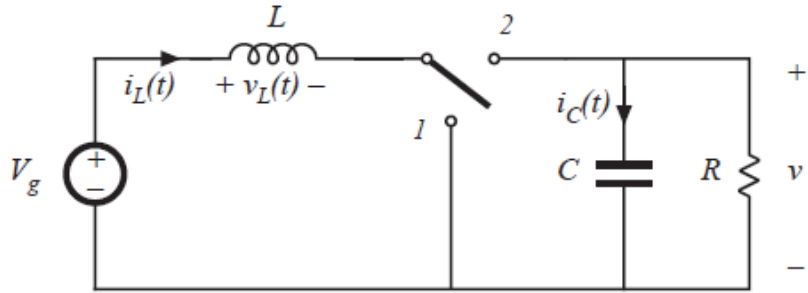

$$V_g = 48 \text{ V}$$

$$V = 120 \text{ V}$$

$$P_{\text{out}} = 150 \text{ W}$$

$$f_{\text{sw}} = 100 \text{ kHz}$$

$$\Delta i_L = 20\% I_L$$

$$\Delta v = 100 \text{ mV}$$

Johns Hopkins Engineering

Power Electronics 525.725


Module 2 Lecture 2b

Switch realization, losses, and efficiency of a Switching Converter



SPST (single-pole single-throw) switches

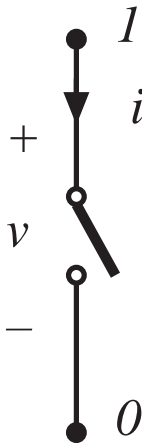
SPST switch, with voltage and current polarities defined




All power semiconductor devices function as SPST switches.

Buck converter

with SPDT switch:

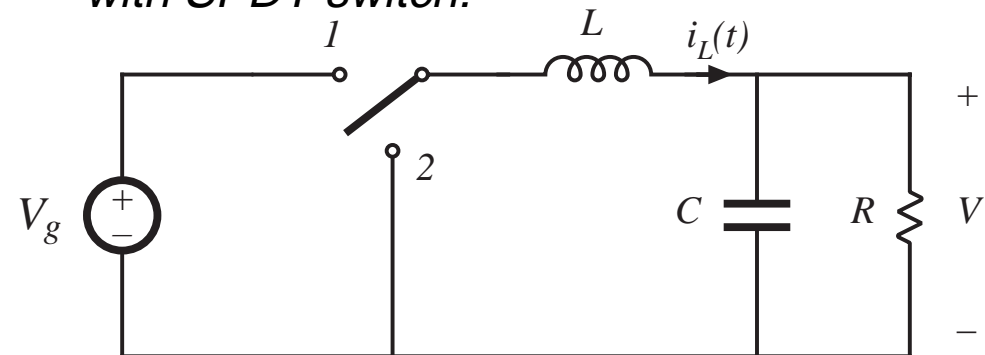



with two SPST switches:

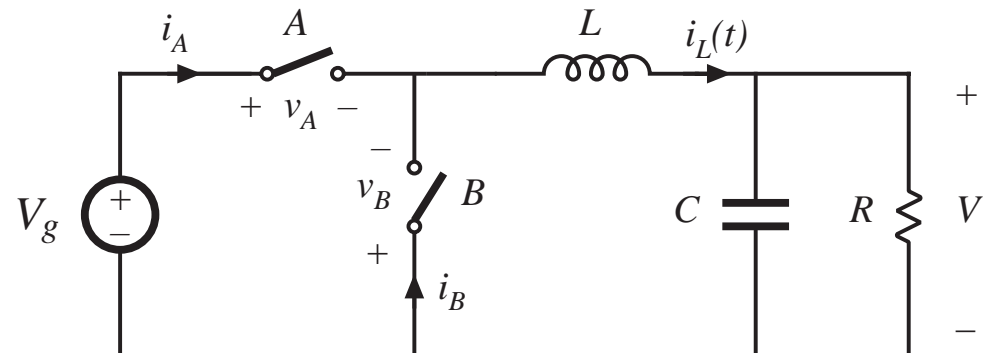

Realization of SPDT switch using two SPST switches

- A nontrivial step: two SPST switches are not exactly equivalent to one SPDT switch
- It is possible for both SPST switches to be simultaneously ON or OFF
- Behavior of converter is then significantly modified
—discontinuous conduction modes (ch. 5)
- Conducting state of SPST switch may depend on applied voltage or current —for example: diode

Quadrants of SPST switch operation

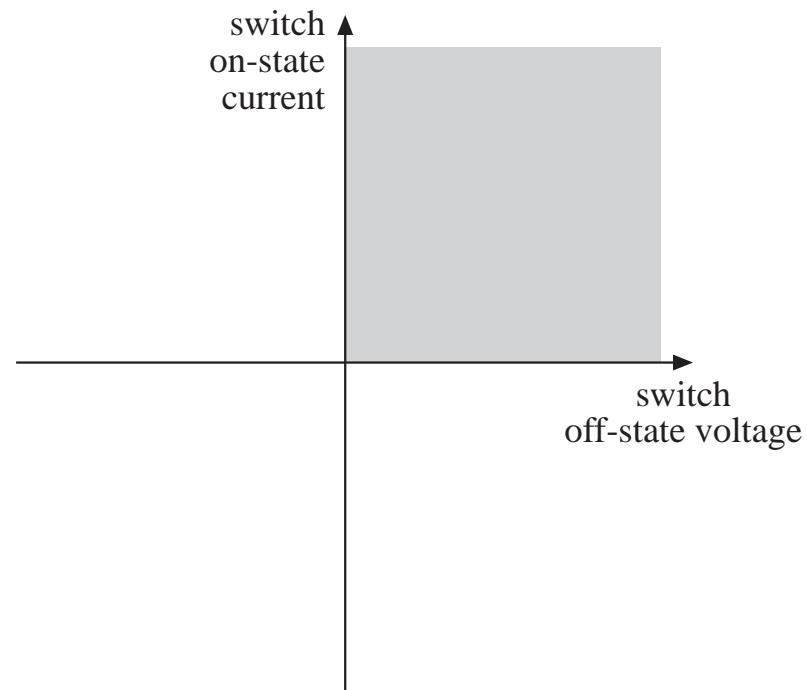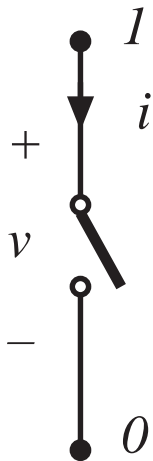


A single-quadrant switch example:

ON-state: $i > 0$


OFF-state: $v > 0$

Some basic switch applications


Single-quadrant switch

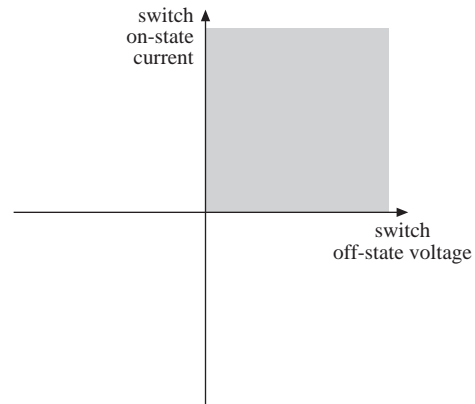

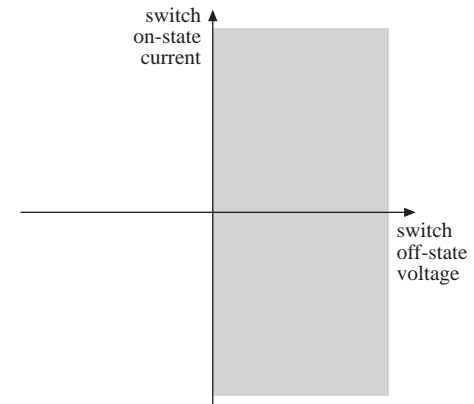
Current-bidirectional two-quadrant switch



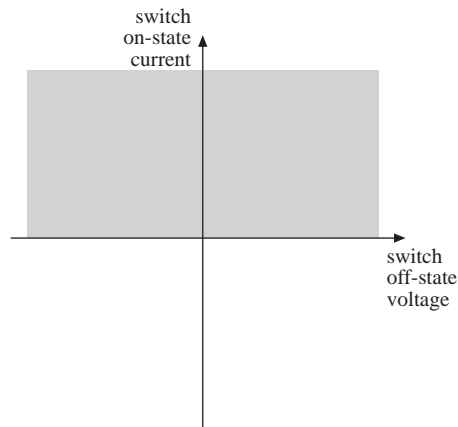
Voltage-bidirectional two-quadrant switch



Four-quadrant switch

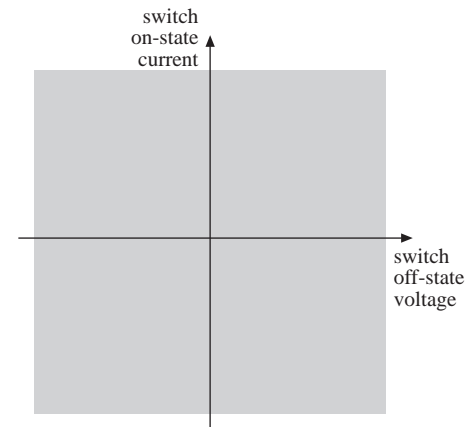

4.1.1. Single-quadrant switches

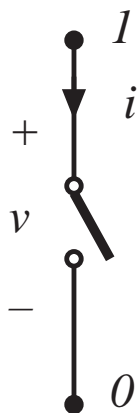


Active switch: Switch state is controlled exclusively by a third terminal (control terminal).

Passive switch: Switch state is controlled by the applied current and/or voltage at terminals 1 and 2 .


SCR: A special case — turn-on transition is active, while turn-off transition is passive.

Single-quadrant switch: on-state $i(t)$ and off-state $v(t)$ are unipolar.

The diode

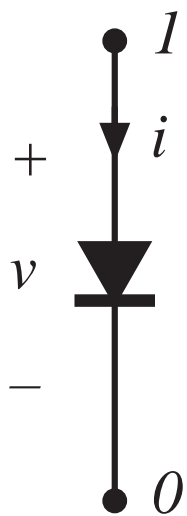

Symbol

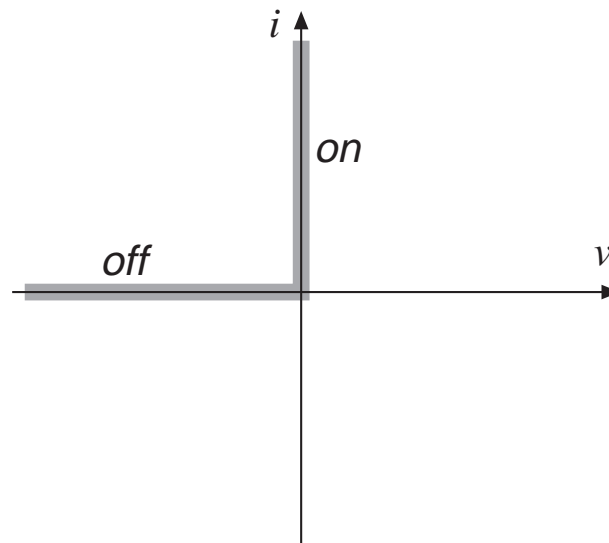


instantaneous i - v characteristic



- *A passive switch*
- *Single-quadrant switch:*
- *can conduct positive on-state current*
- *can block negative off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the diode i - v characteristic, then switch can be realized using a diode*

The Bipolar Junction Transistor (BJT) and the Insulated Gate Bipolar Transistor (IGBT)

BJT

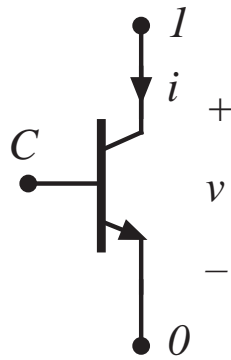


IGBT

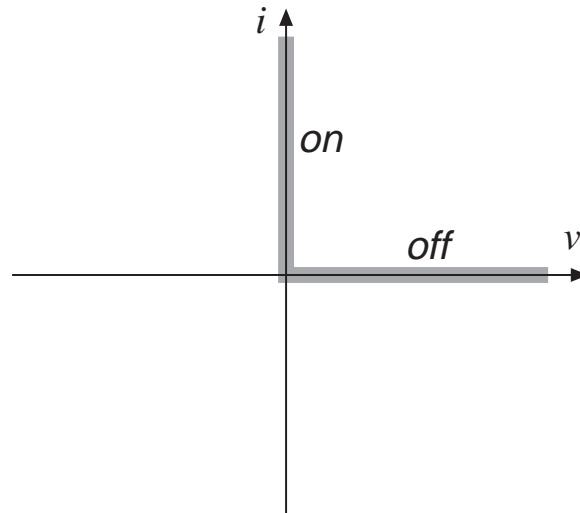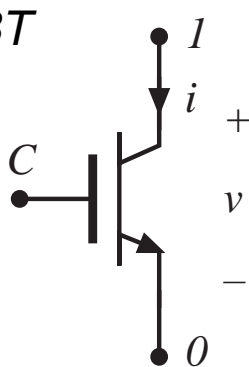

instantaneous i - v characteristic

- *An active switch, controlled by terminal C*
- *Single-quadrant switch:*
- *can conduct positive on-state current*
- *can block positive off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the transistor i - v characteristic, then switch can be realized using a BJT or IGBT*

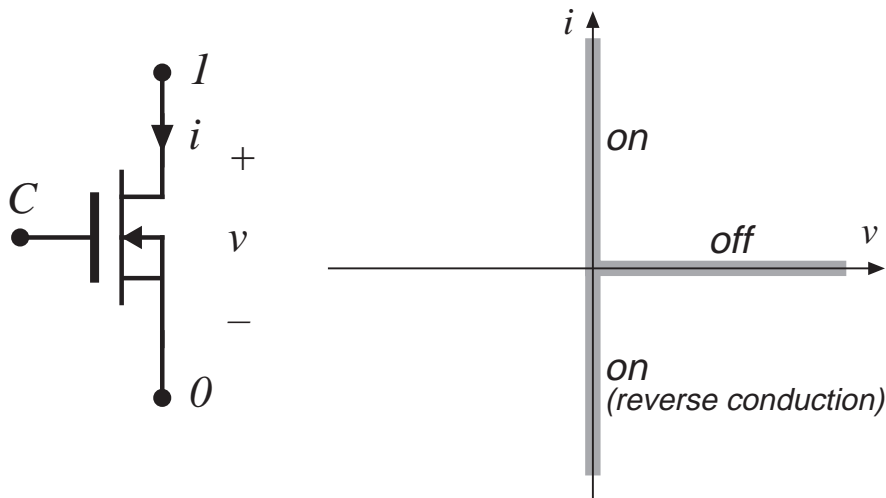The Metal-Oxide Semiconductor Field Effect Transistor (MOSFET)




Symbol instantaneous i - v characteristic

- *An active switch, controlled by terminal C*
- *Normally operated as single-quadrant switch:*
- *can conduct positive on-state current (can also conduct negative current in some circumstances)*
- *can block positive off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the MOSFET i - v characteristic, then switch can be realized using a MOSFET*

Realization of switch using transistors and diodes



Buck converter example

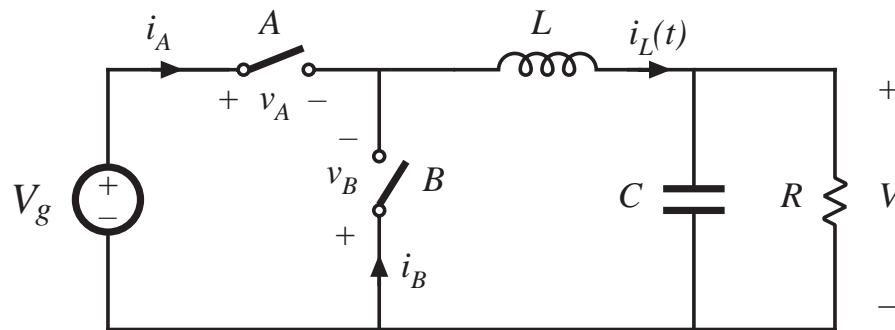




Switch A: transistor

Switch B: diode

*SPST switch
operating points*

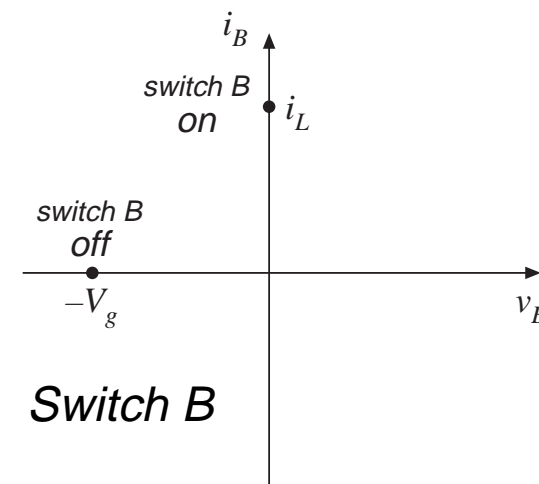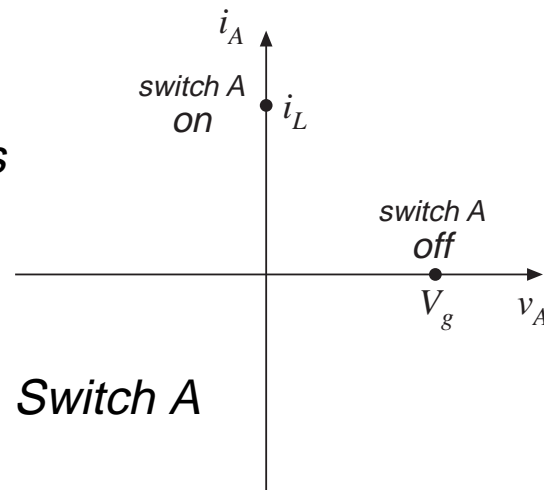


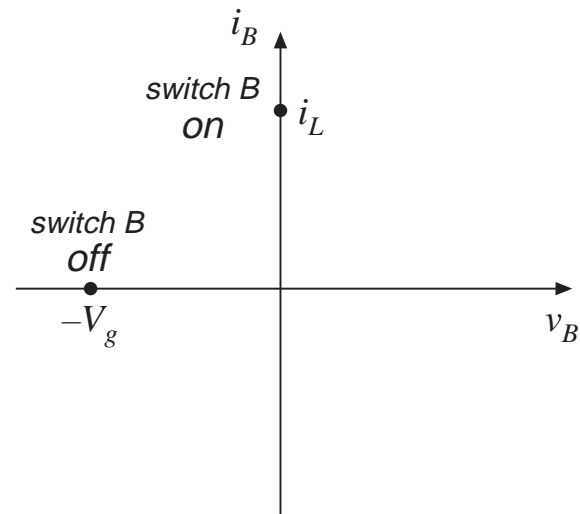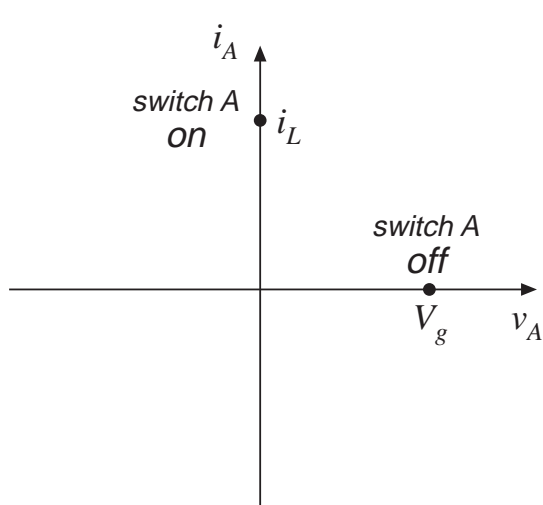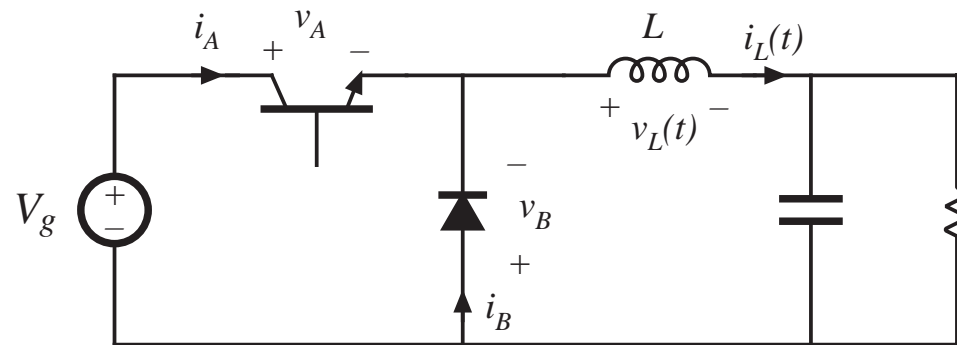Realization of buck converter using single-quadrant switches




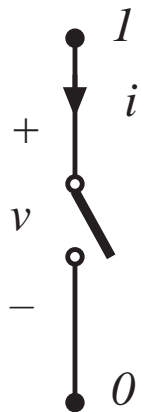4.1.5. Synchronous rectifiers


Replacement of diode with a backwards-connected MOSFET,
to obtain reduced conduction loss




ideal switch

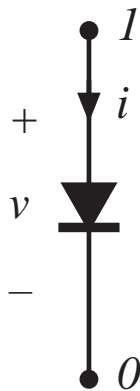

*conventional
diode rectifier*

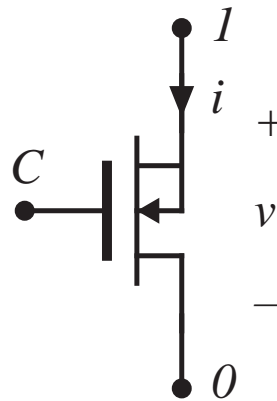


*MOSFET as
synchronous
rectifier*

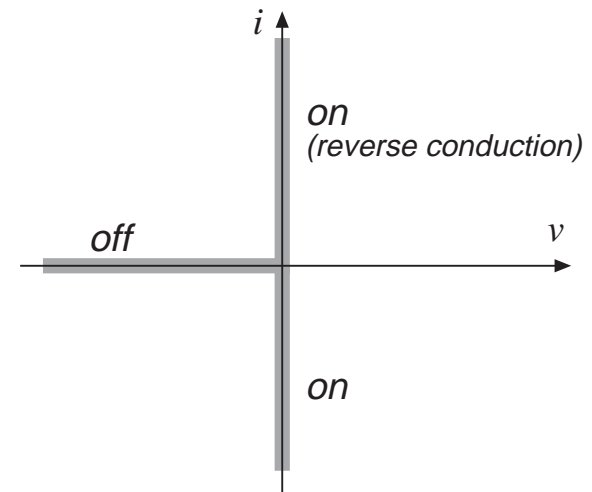

*instantaneous i - v
characteristic*

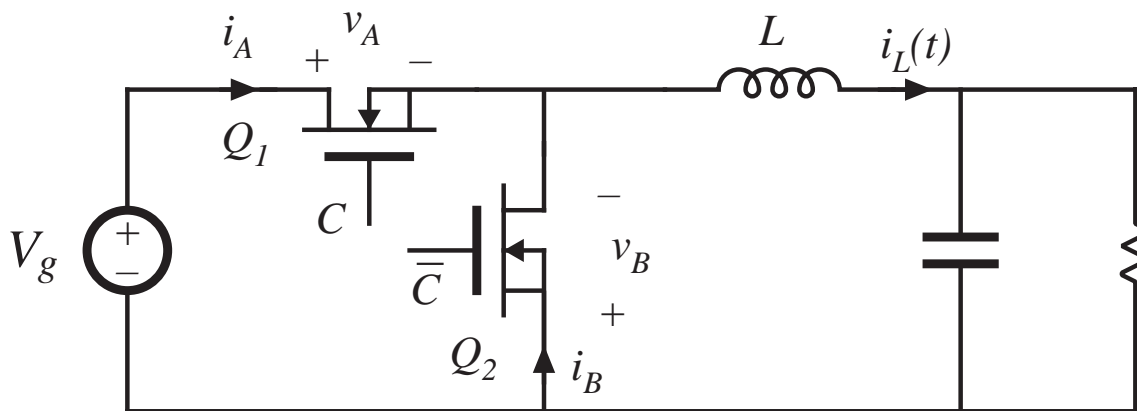Buck converter with synchronous rectifier



- MOSFET Q_2 is controlled to turn on when diode would normally conduct
- Semiconductor conduction loss can be made arbitrarily small, by reduction of MOSFET on-resistances
- Useful in low-voltage high-current applications

Converter Efficiency

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_{out} I_{out}}{V_{out} I_{out} + P_{loss}}$$

$$P_{loss} = P_{sw-cond} + P_{sw-switch} + P_{ind-core} + P_{ind-copper}$$

$P_{sw-switch}$: Switching loss of device

$P_{sw-cond}$: Conduction loss of device

$P_{ind-core}$: Inductor core loss

$P_{ind-copper}$: Inductor copper "conduction" loss

Device Loss Contributors


1. **Switching Loss** – Energy is lost during the “**main**” semiconductor switching transitions, via several mechanisms
 - Transistor switching times “Cross-over” loss
 - Diode stored charge “diode recovery” loss”
 - Energy stored in device capacitances “ CV^2 ” loss
2. **Conduction Loss** -
 - $I^2 \times R$ loss in MOSFET
 - $V_{on} \times I$ loss in IGBT and diode

Main Switch:

An active switch which charges or stores energy in the inductor.



Free Wheel Switch:

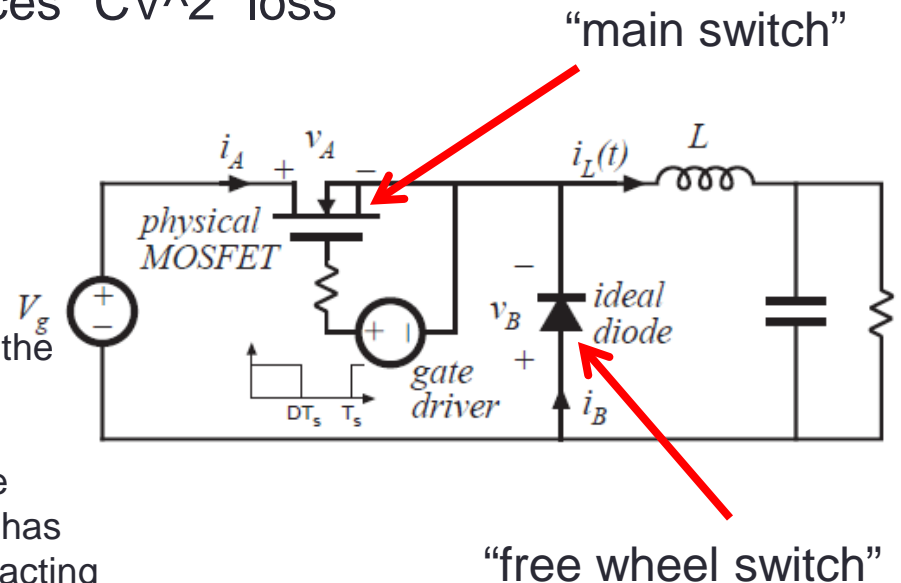The free wheel switch is the switch which keeps the current flowing in an inductor once the main switch has turned off and is typically a diode rectifier or switch acting as a synchronous rectifier.



In General, we will only consider switching loss in the main switch and conduction loss in the main and free wheel switch

MOSFET Data Sheet Capacitances

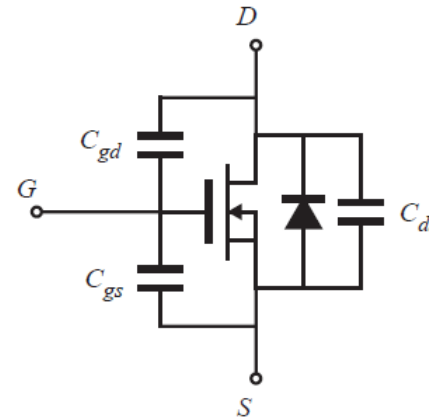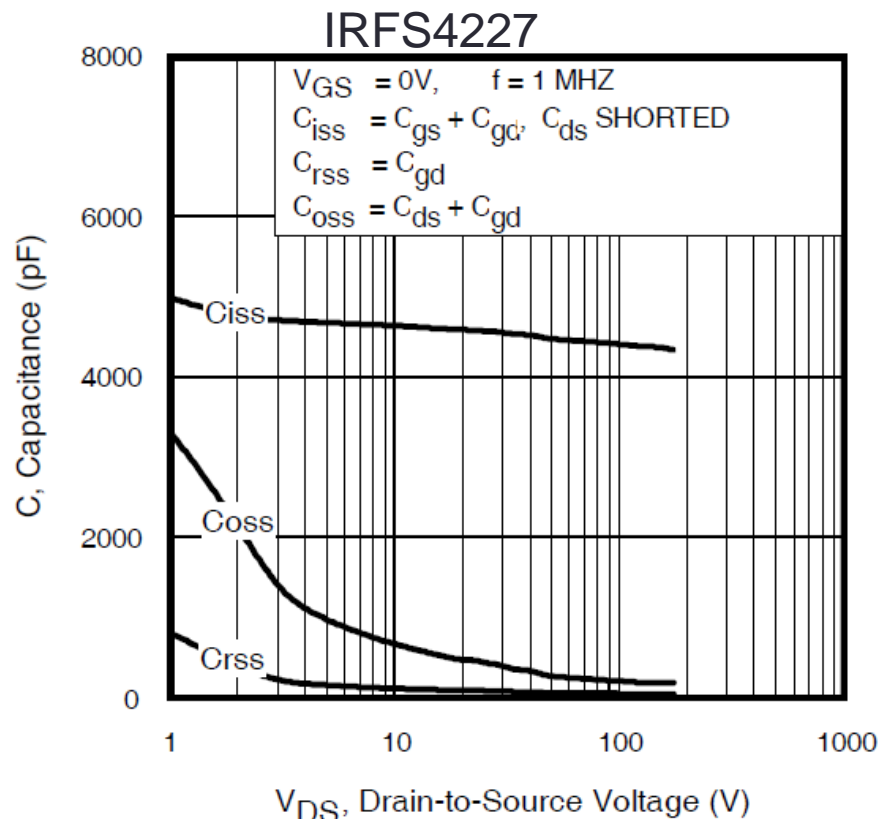

$$C_{iss} = C_{GS} + C_{GD}, C_{DS} \text{ Shorted}$$



$$C_{rss} = C_{GD} \text{ "Miller Capacitance"}$$

$$C_{oss} = C_{DS} + C_{GD}$$

C_{oss} and C_{rss} VERY nonlinear!!

C_{iss}	Input Capacitance	—	4600	—	pF	$V_{GS} = 0V$
C_{oss}	Output Capacitance	—	460	—		$V_{DS} = 25V$
C_{rss}	Reverse Transfer Capacitance	—	91	—		$f = 1.0\text{MHz.}$
$C_{oss \text{ eff.}}$	Effective Output Capacitance	—	360	—		$V_{GS} = 0V, V_{DS} = 0V \text{ to } 160V$

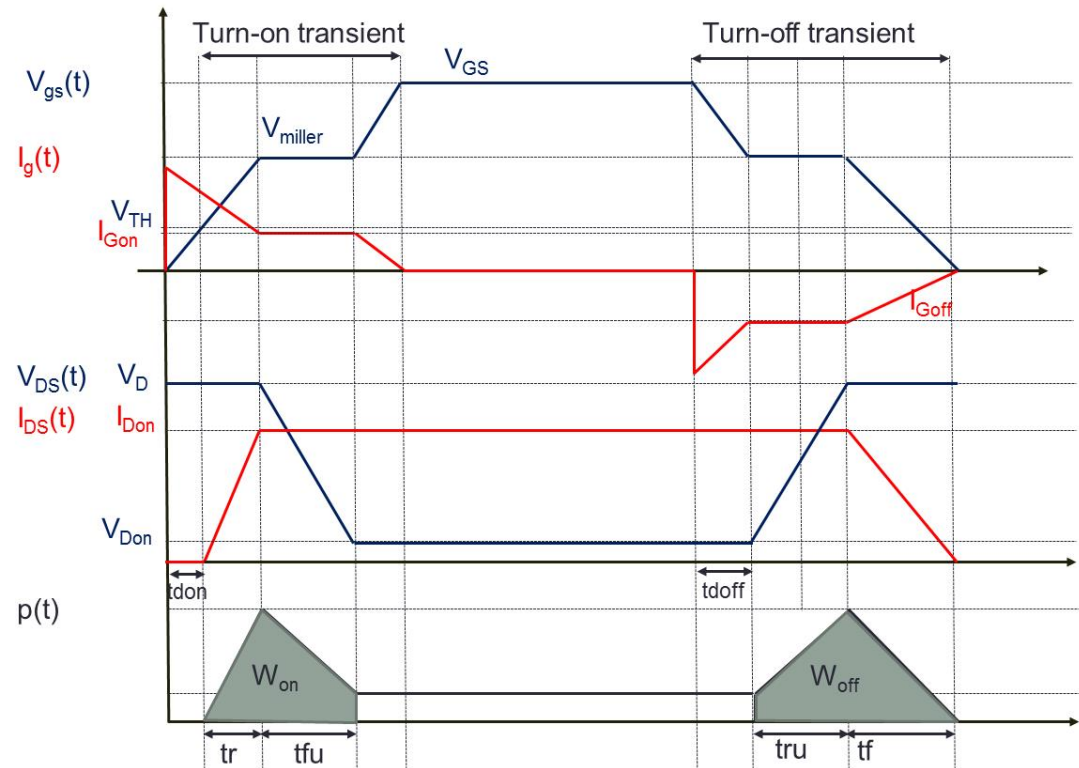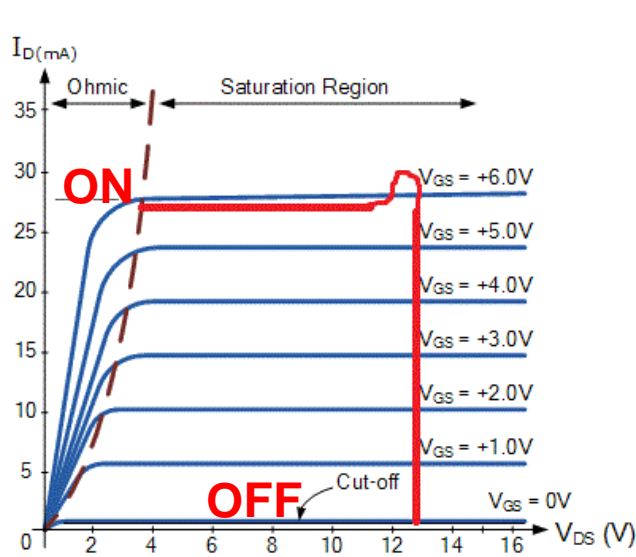MOSFET Switching Loss -MOSFET OFF to ON Trajectory



V_D : Main Device Blocking Voltage

V_{Don} : Main Device on-state voltage

V_{TH} : Main Device threshold voltage "voltage at which device starts to conduct"

t_{don} : The time it takes for the gate to source voltage to reach the threshold voltage

V_{GS} : Peak applied gate to source voltage

$p(t)$: Instantaneous power dissipation " $V_{DS}(t) \times I_{DS}(t)$ "

I_{Don} : Main Switch Peak Current "average inductor current"

"assume small ripple approximation for main device current when calculating switching loss"

Calculating Miller and Threshold Voltage

1. Pick two points from curve.
Select the drain current values corresponding to vertical lines (less error)
2. Read corresponding gate-to-source voltages on the horizontal axis
3. Calculate miller voltage and threshold voltages and adjust for temperature per the formulas:


$$I_{D1} = K \cdot (V_{GS1} - V_{TH})^2$$

$$I_{D2} = K \cdot (V_{GS2} - V_{TH})^2$$


Solve for K and V_{TH}

$$V_{miller} = V_{TH} + \sqrt{\frac{I_{load}}{K}}$$
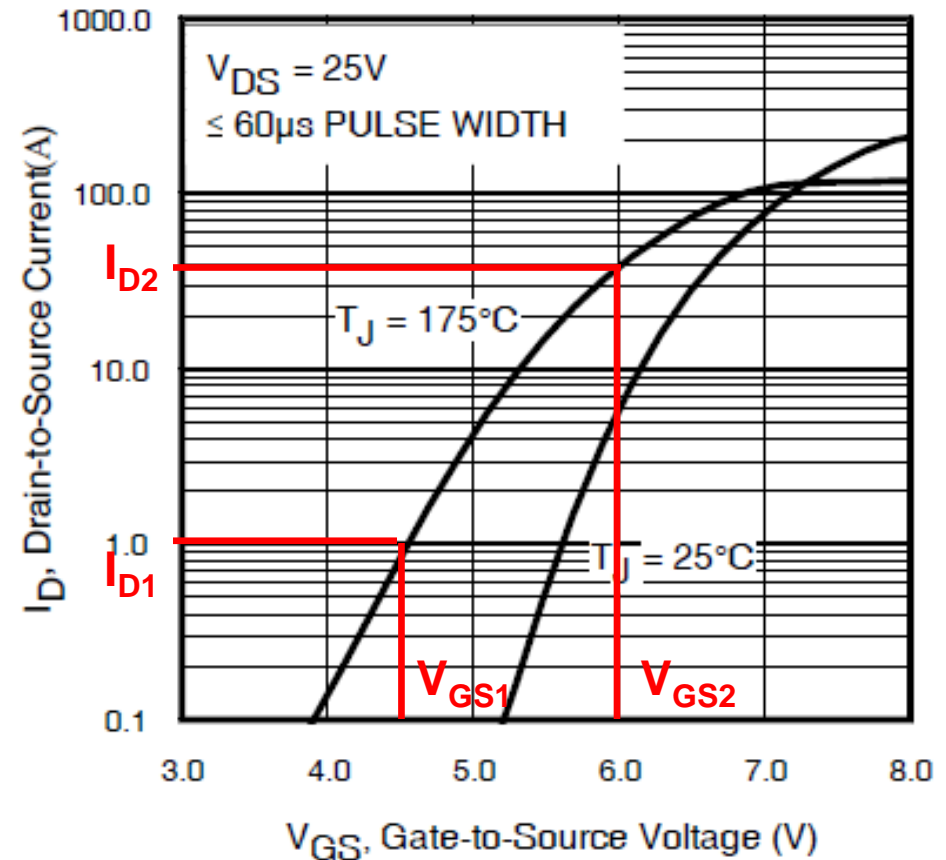
$$\Delta V_{ADJ} = (T_j - T_{curve}) \cdot T_C$$



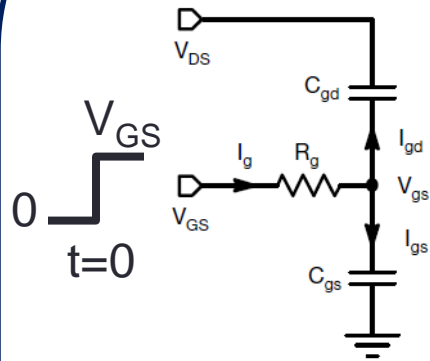MOSFET Switching Loss – Determine Cross-over time



Determine t_{don} and t_r :

$$I_g(t) = \frac{V_{GS} - V_{gs}(t)}{R_g}$$

$$I_g(t) = I_{gs}(t) + I_{gd}(t)$$

$$I_{gs}(t) = C_{gs} \frac{dV_{gs}(t)}{dt}$$

$$I_{gd}(t) = C_{gd} (V_{DS}) \frac{d(V_{gs}(t) - V_{DS}(t))}{dt}$$


Since $V_{DS}(t)$ is constant during this interval

$$I_{gd}(t) = C_{gd} (V_{DS}) \frac{dV_{gs}(t)}{dt} \Rightarrow I_g(t) = (C_{gs} + C_{gd} (V_{DS})) \frac{dV_{gs}(t)}{dt}$$

$$I_g(t) = (C_{gs} + C_{gd} (V_{DS})) \frac{dV_{gs}(t)}{dt}$$


Solving ode

$$V_{gs}(t) = V_{GS} \left(1 - e^{-\frac{t}{R_g C_{iss}|V_{DS}}} \right)$$

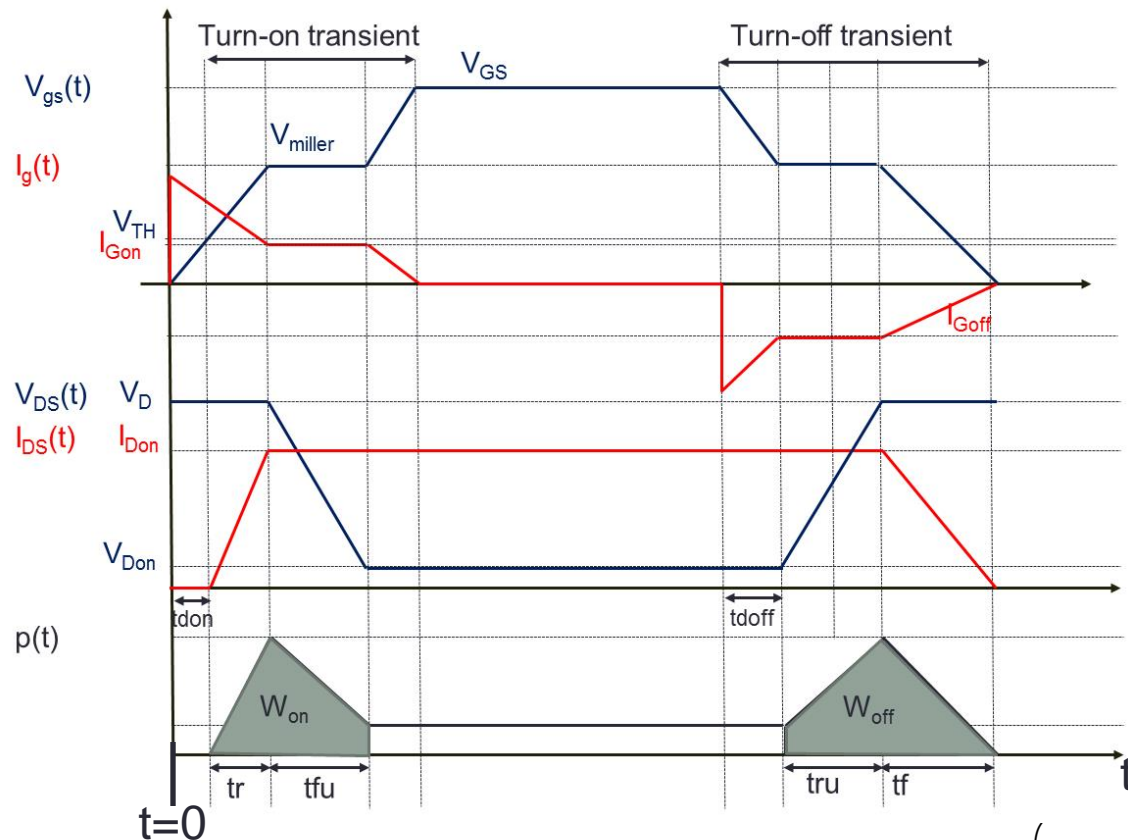

$$t = R_g C_{iss}|V_{DS} \ln \left(\frac{1}{1 - \frac{V_{gs}(t)}{V_{GS}}} \right)$$

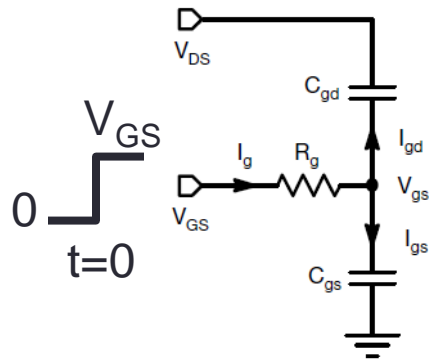MOSFET Switching Loss – Determine Cross-over time cont.




Determine t_{don} and t_r :

$$t_{don} = R_g C_{iss}|_{V_D} \ln \left(\frac{1}{1 - \frac{V_{TH}}{V_{GS}}} \right)$$

$$t_{don} + t_r = R_g C_{iss}|_{V_D} \ln \left(\frac{1}{1 - \frac{V_{miller}}{V_{GS}}} \right)$$

$$t_r = R_g C_{iss}|_{V_D} \ln \left(\frac{1}{1 - \frac{V_{miller}}{V_{GS}}} \right) - R_g C_{iss}|_{V_D} \ln \left(\frac{1}{1 - \frac{V_{TH}}{V_{GS}}} \right)$$

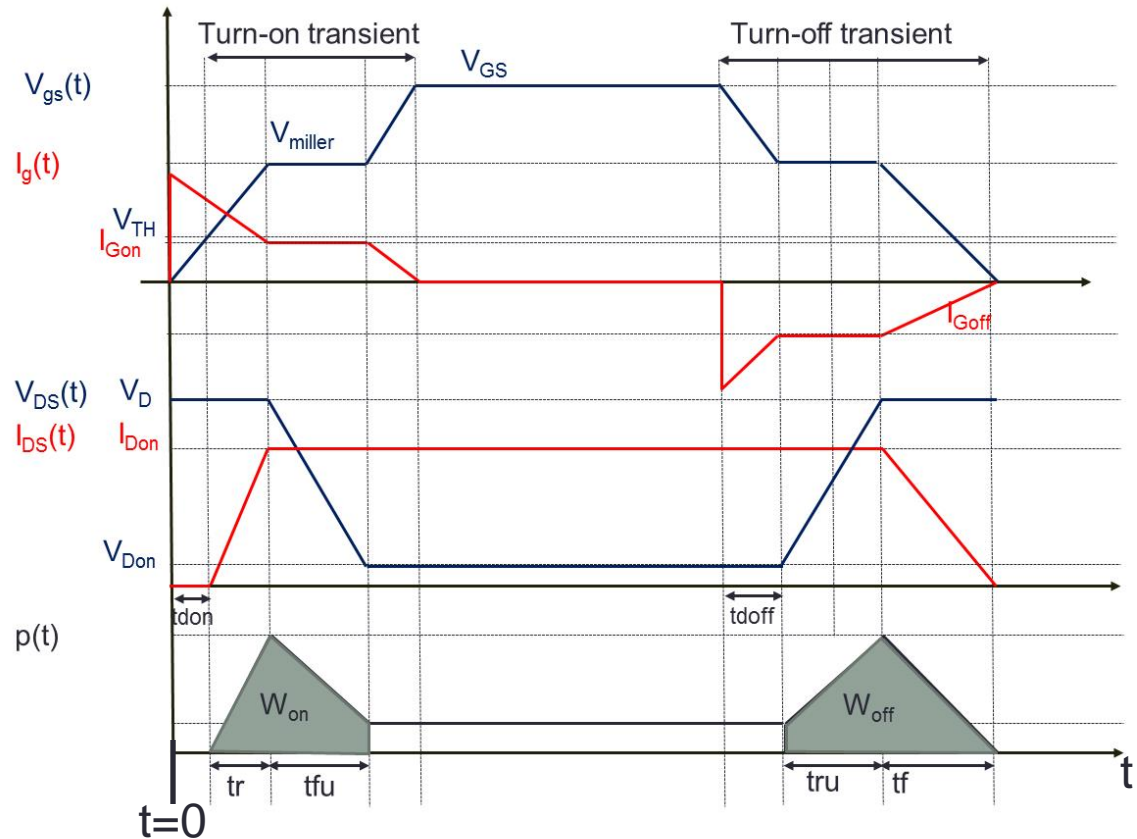

Similarly for t_{doff} and t_f :

$$t_{doff} = R_G C_{iss}|_{V_{Don}} \ln \left(\frac{V_{GS}}{V_{miller}} \right)$$

$$t_f = R_G C_{iss}|_{V_D} \ln \left(\frac{V_{miller}}{V_{TH}} \right)$$

MOSFET Switching Loss – Determine Cross-over time cont.

Determine t_{fu} and recall C_{gs} is a function of V_{DS} :

$$I_g(t) = \frac{V_{GS} - V_{gs}(t)}{R_g} = \frac{V_{GS} - V_{miller}}{R_g} = I_{Gon}$$

$$I_g(t) = I_{gs}(t) + I_{gd}(t) = C_{gd}(V_{DS}) \frac{d(V_{gs}(t) - V_{DS}(t))}{dt}$$

Since $V_{gs}(t)$ is constant during interval

$$\frac{V_{GS} - V_{miller}}{R_g} = -C_{gd}(V_{DS}) \frac{dV_{DS}(t)}{dt}$$

C_{gd} is a function of V_{DS} !!



$$\int_{t_{fu}} \frac{V_{GS} - V_{miller}}{R_g} dt = \int_{V_D}^{V_{Don}} -C_{gd}(V_{DS}) dV_{DS} = \int_{V_{Don}}^{V_D} C_{gd}(V_{DS}) dV_{DS}$$

$$\frac{V_{GS} - V_{miller}}{R_g} t_{fu} = \int_{V_{Don}}^{V_D} C_{gd}(V_{DS}) dV_{DS}$$

$$t_{fu} = \frac{R_g \int_{V_{Don}}^{V_D} C_{gd}(V_{DS}) dV_{DS}}{V_{GS} - V_{miller}}$$

Similarly for t_{ru} :
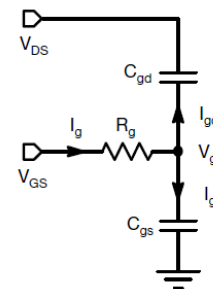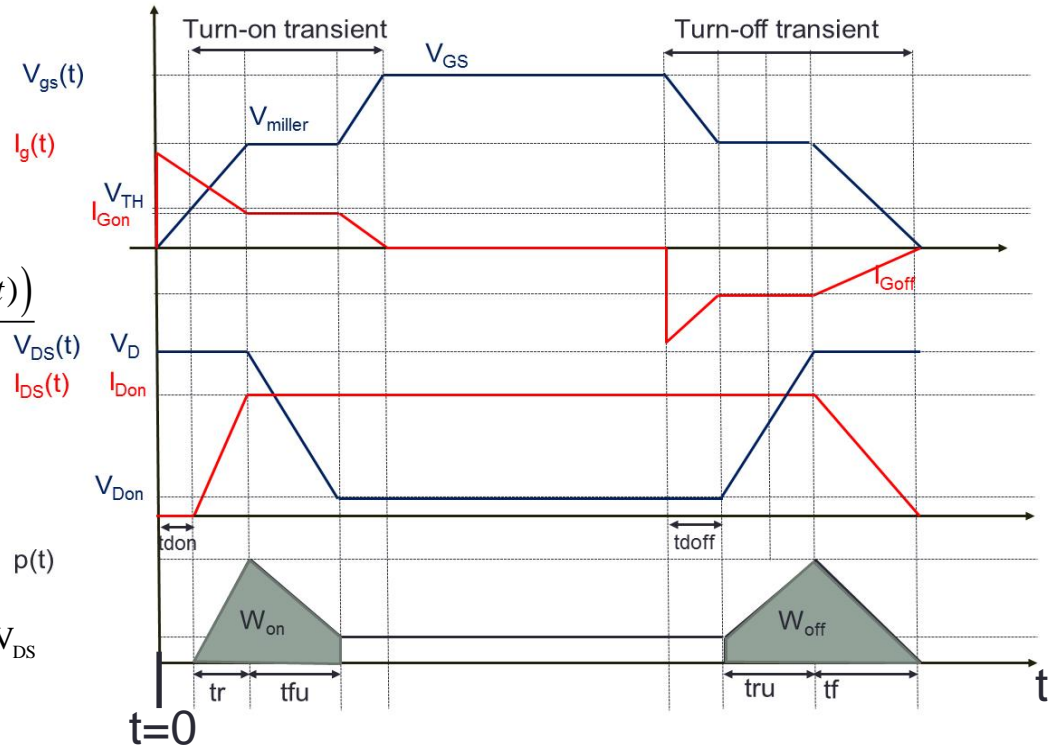
$$t_{ru} = \frac{R_g \int_{V_{Don}}^{V_D} C_{gd}(V_{DS}) dV_{DS}}{V_{miller}}$$




Cross-over Switching Energy:

$$W_{on} = \frac{1}{2} t_r V_D I_{Don} + \frac{1}{2} t_{fu} V_D I_{Don}$$


$$W_{off} = \frac{1}{2} t_{ru} V_D I_{Don} + \frac{1}{2} t_f V_D I_{Don}$$

Diode Reverse Recovery

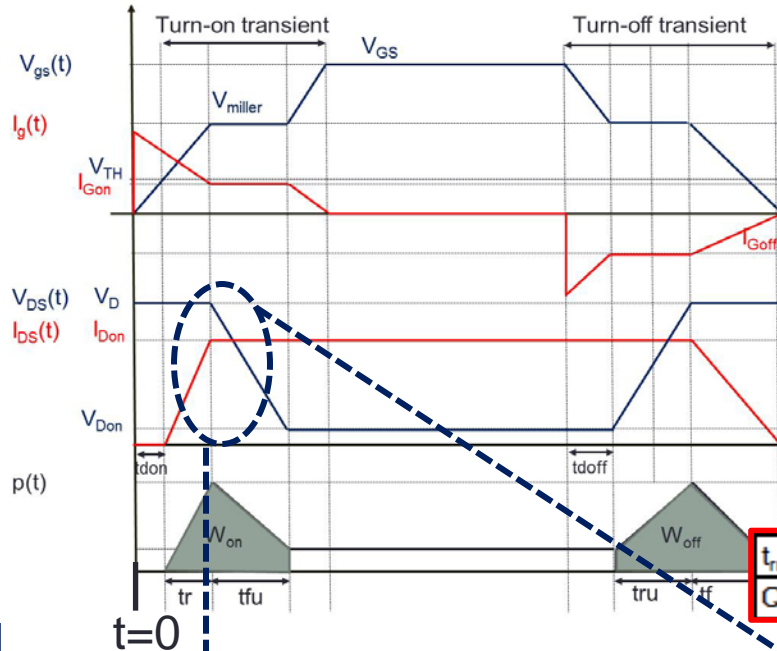

- Reverse Recovery Time (t_{rr}) and Recovery Charge (Q_{rr}) from datasheet
- Diode recovery stored charge Q_{rr} flows through transistor during turn-on, inducing additional loss in MOSFET
- Diode does not block voltage until peak reverse recovery current has been reached

t_{rr}	Reverse Recovery Time	—	100	150	ns
Q_{rr}	Reverse Recovery Charge	—	430	640	nC

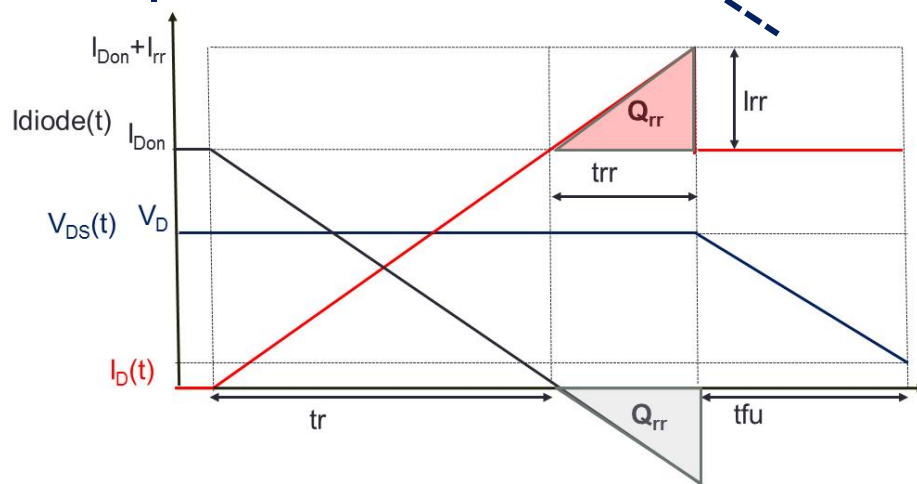

Reverse Recovery Induced Energy

$$i_{diode}(t) = \frac{dQ}{dt}$$


$$\int_{t_{rr}} i_{diode}(t) dt = \int_0^{Q_{rr}} dQ$$

$$\int_{t_{rr}} i_{diode}(t) dt = \frac{1}{2} t_{rr} I_{rr} = Q_{rr} \Rightarrow I_{rr} = \frac{2Q_{rr}}{t_{rr}}$$

$$W_{rr} = \frac{1}{2} t_{rr} I_{rr} V_D + V_D I_{Don} t_{rr} = Q_{rr} V_D + V_D I_{Don} t_{rr}$$

MOSFET Output Capacitance “CV² Loss”

Buck converter example

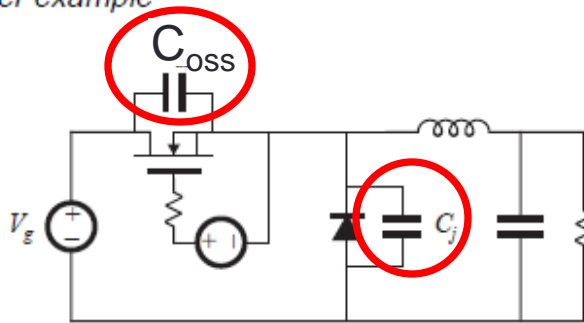

- Capacitances that appear effectively in parallel with switch elements are shorted when the switch turns on. Their stored energy is lost during the switch turn-on transition.

During the switching transition, C_{oss} and C_j are effectively in parallel. The energy lost when the MOSFET turns on is:

$$W_c = \frac{1}{2} (C_{oss(er)} + C_{j(er)}) (V_D^2 - V_{Don}^2)$$

Where effective energy related capacitors $C_{oss(er)}$, $C_{j(er)}$ are linear capacitors with same energy stored at V_D as nonlinear capacitors $C_{oss}(v_{ds})$, $C_j(v_{ds})$

$$C_{oss(er)} = 2 \frac{\int_{V_{Don}}^{V_D} C_{oss}(v_{ds}) v_{ds} dv_{ds}}{(V_D^2 - V_{Don}^2)}$$

$$C_{j(er)} = 2 \frac{\int_{V_{Don}}^{V_D} C_j(v_{ds}) v_{ds} dv_{ds}}{(V_D^2 - V_{Don}^2)}$$

$$W_c = \frac{1}{2} \left(2 \frac{\int_{V_{Don}}^{V_D} C_{oss}(v_{ds}) v_{ds} dv_{ds}}{(V_D^2 - V_{Don}^2)} + 2 \frac{\int_{V_{Don}}^{V_D} C_j(v_{ds}) v_{ds} dv_{ds}}{(V_D^2 - V_{Don}^2)} \right) (V_D^2 - V_{Don}^2)$$

Calculate Total MOSFET Switching Loss

$$p_{sw}(t) = i_{sw}(t) \cdot v_{sw}(t)$$

$$W_{sw} = \int_{T_{sw}} i_{sw}(t) \cdot v_{sw}(t) dt$$

$$p_{sw-avg} = \frac{1}{T_{sw}} W_{sw} = f_{sw} W_{sw}$$

The switching loss is directly proportional to the switching frequency

$$W_{m-sw} = \underbrace{W_{on} + W_{off}}_{\text{crossover}} + \underbrace{W_{rr}}_{\text{diode recovery}} + \underbrace{W_c}_{CV^2}$$

$$W_{on} = \frac{1}{2} t_r V_D I_{Don} + \frac{1}{2} t_{fu} V_D I_{Don}$$

$$W_{off} = \frac{1}{2} t_{ru} V_D I_{Don} + \frac{1}{2} t_f V_D I_{Don}$$

$$W_{rr} = Q_{rr} V_D + V_D I_{Don} t_{rr}$$

$$W_c = \frac{1}{2} (C_{oss(er)} + C_{j(er)}) (V_D^2 - V_{Don}^2)$$

$$p_{sw-avg} = W_{m-sw} f_{sw}$$

MOSFET Conduction Loss


- After MOSFET is fully turned on, it behaves as a resister, given by R_{dson}

$$v_{ds}(t) = i(t) \cdot R_{dson}$$

$$p_c(t) = i(t)^2 \cdot R_{dson}$$

$$p_{c-avg} = \frac{1}{T_{sw}} \left(\int_0^{DT_{sw}} i(t)^2 \cdot R_{dson} dt + \int_{DT_{sw}}^{T_{sw}} 0 dt \right)$$

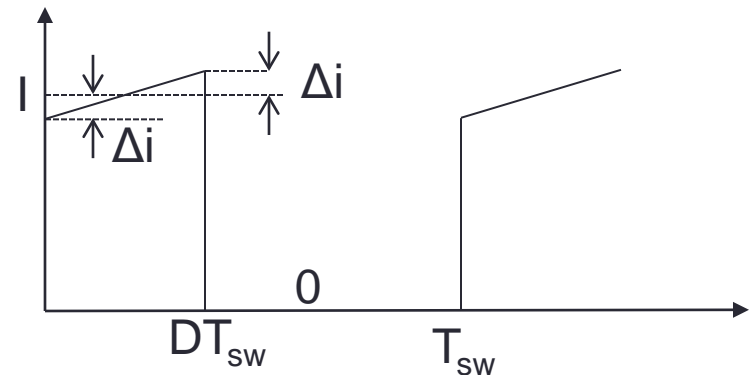Typical Switch Current waveform during conduction



$$p_{c-avg} = \frac{1}{T_{sw}} \left(\int_0^{DT_{sw}} \left((I - \Delta i) + \frac{2\Delta i}{DT_{sw}} t \right)^2 \cdot R_{dson} dt + \int_{DT_{sw}}^{T_{sw}} 0 dt \right)$$

$$p_{c-avg} = \frac{1}{3} R_{dson} D (3I^2 + \Delta i^2)$$


in general:

$$p_{c-avg} = I_{rms}^2 R_{dson}$$

can also use simulation to calculate rms current in switch

Diode Loss – Conduction Loss only

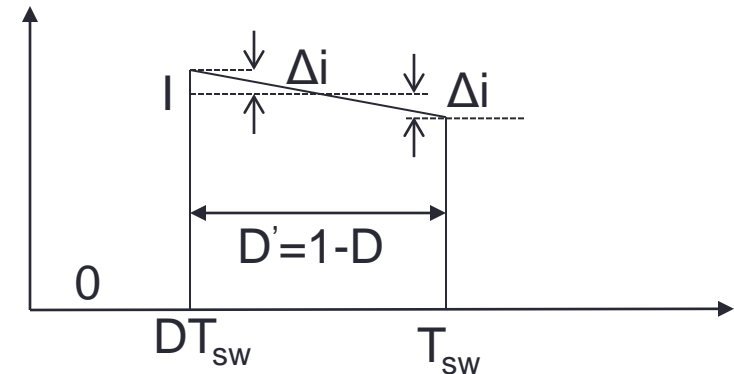- Diode turns on without cross over loss in most cases
- Majority loss in diode comes from conduction loss
- Reverse recovery loss is induced in the adjacent switch



$$v_{diode}(t) = v_{on}$$

$$p_{cd}(t) = i(t) \cdot v_{on}$$

$$p_{cd-avg} = \frac{1}{T_{sw}} \left(\int_0^{DT_{sw}} 0 dt + \int_{DT_{sw}}^{T_{sw}} i(t) \cdot v_{on} dt \right)$$

$$p_{cd-avg} = \frac{1}{T_{sw}} \left(\int_0^{DT_{sw}} 0 dt + \int_{DT_{sw}}^{T_{sw}} \left(I + \Delta i - \left(\frac{2\Delta i}{D'T_{sw}} \right) (t - DT_{sw}) \right) \cdot v_{on} dt \right)$$

$$p_{cd-avg} = (1 - D) I v_{on}$$

Total Loss Summary

- MOSFET Total loss
 - Switching
 - Conducting
- Diode Total loss
 - Conducting
- If using MOSFET in replace of free-wheel diode
 - Conducting $(I_{rms}^2)R_{dson}$

$$P_{mloss} = P_{sw-avg} + P_{c-avg}$$

$$P_{dloss} = \cancel{P_{sw-avg}}^0 + P_{cd-avg}$$

Converter Efficiency

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_{out} I_{out}}{V_{out} I_{out} + P_{loss}}$$

$$P_{loss} = P_{sw-cond} + P_{sw-switch} + P_{ind-core} + P_{ind-copper}$$

$$P_{sw-switch} : \text{Switching loss of device} = p_{sw-avg}$$

$$P_{sw-cond} : \text{Conduction loss of device} = p_{c-avg} + p_{cd-avg}$$

$$P_{ind-core} : \text{Inductor core loss}$$

$$P_{ind-copper} : \text{Inductor copper "conduction" loss}$$

Inductor Loss

- Inductor Copper “conduction” loss

$$P_{ind-copper} = I_{ind-rms}^2 \times R_{ind-esr} \quad (\text{esr-Equivalent series resistance})$$

$$I_{ind-rms} = I \sqrt{1 + \frac{1}{3} \left(\frac{\Delta i}{I} \right)^2} \quad \text{"Appendix A of Erickson Fig. A.2"}$$

Assume:

$$P_{ind-core} = P_{ind-copper}$$