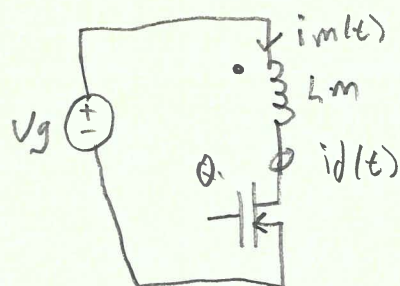


"Flyback in CCM"

On state switch current

"1"



$$i_d(t) = i_m(t)$$

SRA

$$i_d(t) = I_m = \frac{nV}{D'R}$$


b)
$$i_d(t) = \frac{nV}{D'R}$$

+1

Blocking Voltage

1:n
"n1:n2"

"2"

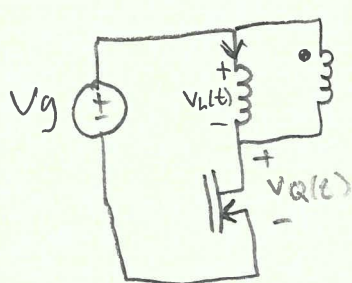

$$-V_g + V_L(t) + V_Q(t) = 0$$

$$V_Q(t) = V_g - V_L(t)$$

$$\frac{V_L(t)}{n_1} = \frac{-V(t)}{n_2}$$

$$V_Q(t) = V_g + \frac{V(t)n_1}{n_2}$$

$$V_Q(t) = V_g + \frac{V(t)}{n}$$

SRA

a)
$$V_Q(t) = V_g + \frac{V}{n}$$



+1

c) If applying small ripple approximation:

$$I_{drms} = \frac{nV}{D'R} \sqrt{D}$$

+0.5



a) "1"

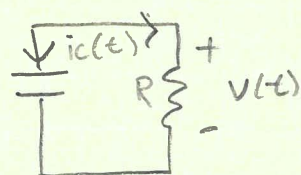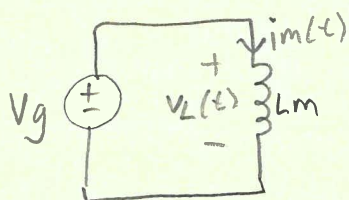

$$\begin{aligned} -V_g + V_L(t) &= 0 \\ V_L(t) &= V_g \\ i_c(t) + \frac{V(t)}{R} &= 0 \\ i_c(t) &= -\frac{V(t)}{R} \end{aligned}$$

SRA $V_L(t) = V_g$
 $i_c(t) = -\frac{V}{R}$

"2"

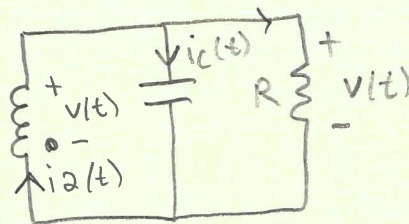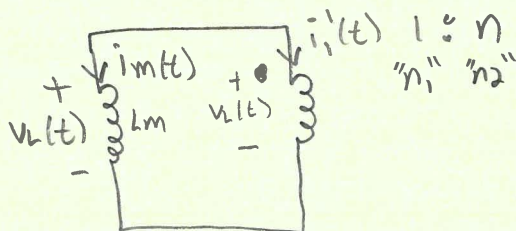

"Transformer" voltage eqn



$$\begin{aligned} \frac{V_L(t)}{n_1} &= -\frac{V(t)}{n_2} \\ V_L(t) &= -\frac{V(t)n_1}{n_2} \\ V_L(t) &= -\frac{V(t)}{n} \end{aligned}$$

$$\begin{aligned} i_2(t) &= i_c(t) + \frac{V(t)}{R} \\ \star i_1'(t)n_1 + i_2(t)n_2 &= 0 \\ i_1'(t) &= -i_m(t) \\ -i_m(t)n_1 + i_2(t)n_2 &= 0 \\ i_2(t) &= \frac{i_m(t)n_1}{n_2} \\ i_2(t) &= \frac{i_m(t)}{n} \\ i_c(t) &= \frac{i_m(t)}{n} - \frac{V(t)}{R} \end{aligned}$$

SRA $V_L(t) = -\frac{V}{n}$

$$i_c(t) = \frac{i_m(t)}{n} - \frac{V}{R}$$

"3"

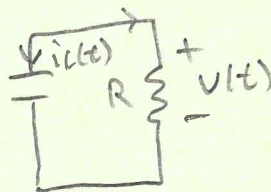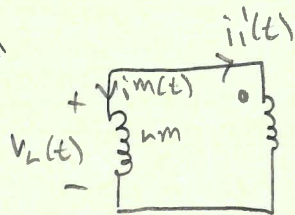

$$\begin{aligned} V_L(t) &= 0 \\ i_c(t) &= -\frac{V(t)}{R} \end{aligned}$$

SRA: $V_L(t) = 0$
 $i_c(t) = -\frac{V}{R}$


a) cont) Volt-Second Balance

$$0 = V_g D_1 + \frac{-V}{n} D_2 + 0(D_3)$$

$$V_g D_1 = \frac{V}{n} D_2$$

$$\frac{V}{V_g} = \frac{D_1}{D_2} n \quad +2$$

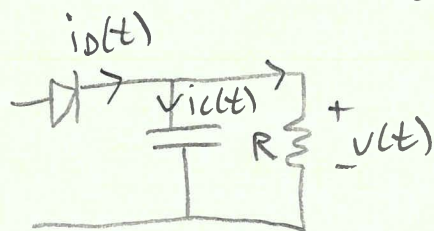
b) In DCM, since you cannot apply SRA, apply charge balance in a manner that results in an expression in terms of average output current "Charge Balance"



$$i_C(t) = i_D(t) - \frac{V(t)}{R}$$

$$\langle i_C(t) \rangle = \langle i_D(t) \rangle - \frac{V}{R} = 0$$

$$\langle i_D(t) \rangle = \frac{V}{R}$$

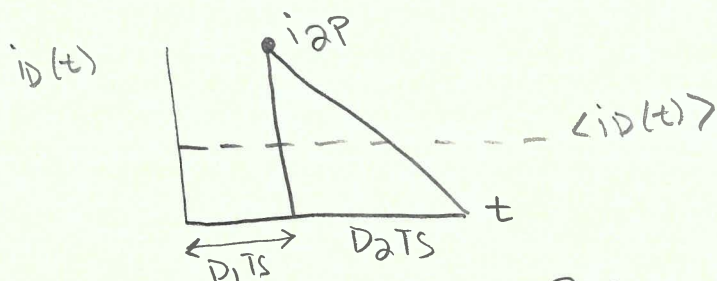

$$\langle i_D(t) \rangle = \frac{1}{T_s} \left[\frac{1}{2} D_2 T_s i_{2P} \right] = \frac{V}{R} \quad (1)$$


$i_2(t)$ relates to $i_1'(t)$ during "2"

$$i_{2P} = i_2(t = D_1 T_s)$$

$$0 = i_1'(t) n_1 + i_2(t) n_2$$

at $t = D_1 T_s$
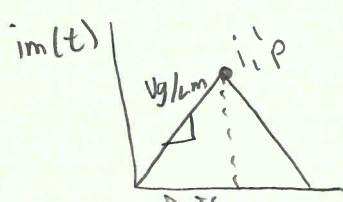
$$0 = -\underbrace{i_{1P}}_{i_1'(t=D_1 T_s)} n_1 + i_2(t = D_1 T_s) n_2$$



$$0 = -i_{1P} n_1 + i_{2P} n_2$$

b cont)


$$i_{1P} = \frac{V_g}{L_m} D_1 T_s$$

$$0 = -\frac{V_g}{L_m} D_1 T_s n_1 + i_{2P} n_2$$

$$i_{2P} = \frac{V_g}{L_m} D_1 T_s \frac{n_1}{n_2} = \frac{V_g}{L_m} \frac{D_1 T_s}{n} \quad (2)$$

Solve (1) + (2) for $i_{2P} + D_2$
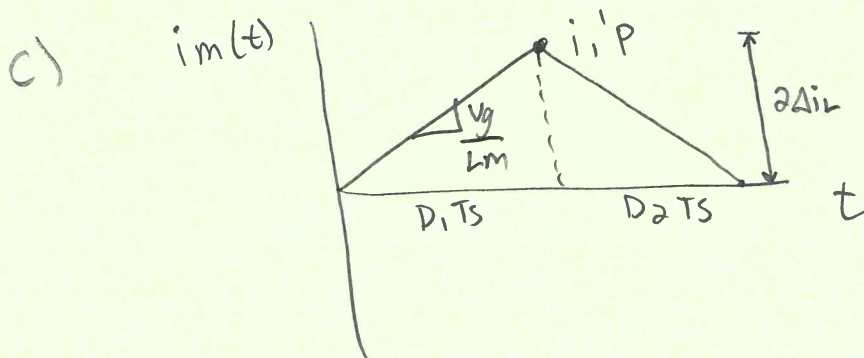
$$+2 \quad D_2 = \frac{2L_m V_n}{D_1 R T_s V_g} ; \quad i_{2P} = \frac{D_1 T V_g}{L_m n}$$



at boundary of CCM/DCM $D_3 = 0$

$$2\Delta i_L = i_{1P} = \frac{V_g}{L_m} D_1 T_s$$

we know at boundary, $\langle i_L(t) \rangle = \frac{nV}{D'R}$

$$\Delta i_L = \langle i_L(t) \rangle$$

$$\frac{V_g}{2L_m} D_1 T_s = \frac{nV}{D'R_{crit}}$$

$$R_{crit} = \frac{2L_m V_n}{D_1 D' T_s V_g}$$

+2

"since still in CCM"
right before DCM

Simulink at critical conduction

$$D_1 = .3333$$

+1.5

$$D_2 = .6667$$

$$i_{peak} = i_{ip} = 0.64 \text{ A}$$

$$R_{crit} = 28.125 \Omega$$

