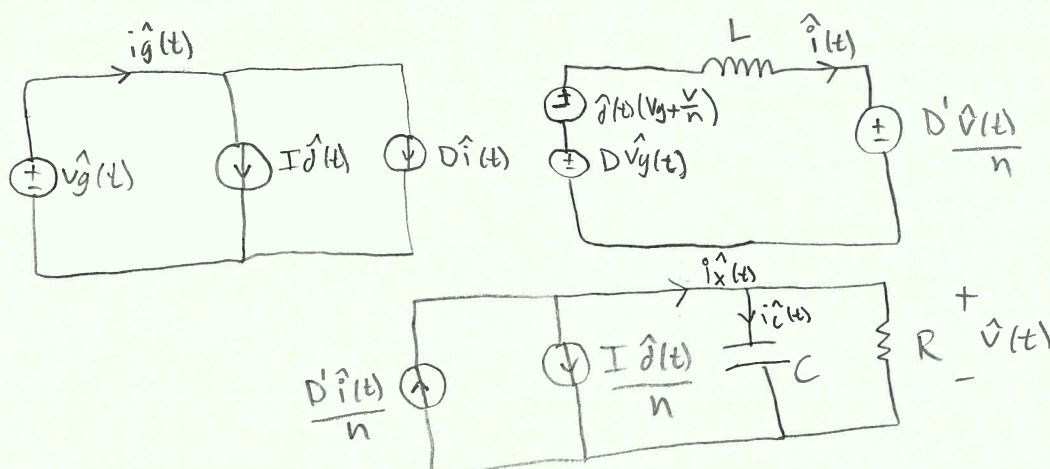


a) Small signal model of flyback "Fig 7.26 Ron $\neq 0$ "



$$Z_n(s) = \frac{\hat{v}_{test}(s)}{\hat{i}_{test}(s)} \Big|_{\hat{v} \rightarrow 0 \text{ null}}$$

if $\hat{v} \rightarrow 0$, then the current through parallel output impedance (R||C) must be zero. This means $\hat{i}_x(s) = 0$. We can do a

KCL

$$\frac{D'\hat{i}(s)}{n} = \frac{I_d(s)}{n} + \hat{i}_x(s) \xrightarrow{0}$$

$$\frac{D'\hat{i}(s)}{n} = \frac{I_d(s)}{n} \quad (1)$$

$$\hat{i}_g(s) = \hat{i}_{test}(s) = I_d(s) + D\hat{i}(s) \quad (2)$$

KVL

$$-D\hat{v}_g(s) + sL\hat{i}(s) + \frac{D'\hat{v}(s)}{n} \xrightarrow{\hat{v} \rightarrow 0 \text{ null}} = \hat{i}(s)(V_g + \frac{V}{n})$$

$$-D\hat{v}_g(s) + sL\hat{i}(s) = \hat{i}(s)(V_g + \frac{V}{n})$$

$$\hat{v}_g(s) = \hat{v}_{test}(s)$$

$$-D\hat{v}_{test}(s) + sL\hat{i}(s) = \hat{i}(s)(V_g + \frac{V}{n}) \quad (3)$$

Solve (1)-(3) for $\hat{v}_{test}(s)$, $\hat{i}(s)$, $\hat{i}_d(s)$

$$Z_n(s) = \frac{\hat{v}_{test}(s)}{\hat{i}_{test}(s)} \Big|_{\hat{v} \rightarrow 0 \text{ null}} = \frac{sLnI - D'Vgn - D'V}{DnI(D' + D)}$$

a cont)

$$Z_n(s) = \frac{sL n I - D' V_{gn} - D' V}{D n I (D' + D)}$$

$$Z_n(s) = \frac{sL n I - D' (V_{gn} + V)}{D n I}$$

DC operating Pts

$$I = \frac{nV}{D'R} = 1.4694 A$$

$$V = \frac{D V_{gn}}{D'} = 10.2857 V$$

$$Z_D(s) = \left. \frac{\hat{v}_{test}(s)}{\hat{i}_{test}(s)} \right|_{\hat{d}(s)=0}$$

$$\hat{v}_g(s) = \hat{v}_{test}(s)$$

KVL

$$-D \hat{v}_{test}(s) + sL \hat{i}(s) + \frac{D' \hat{v}(s)}{n} = 0 \quad (1)$$

$$\hat{i}_g(s) = \hat{i}_{test}(s) = D \hat{i}(s) \quad (2)$$

KCL

$$\frac{D' \hat{i}(s)}{n} = \frac{I \hat{d}(s)}{n} + \hat{i}_x(s)$$

$$\frac{D' \hat{i}(s)}{n} = \hat{i}_x(s) \quad (3)$$

$$\hat{i}_x(s) = \frac{\hat{v}(s)}{\frac{1}{sC}} + \frac{\hat{v}(s)}{R}$$

solve (1)-(4) for $\hat{v}_{test}(s)$, $\hat{i}(s)$, $\hat{i}_x(s)$, $\hat{v}(s)$

$$Z_D(s) = \frac{s^2 L n^2 R C + sL n^2 + R - 2DR + D^2 R}{D^2 n^2 (sCR + 1)}$$

(b1) Design filter for at least 100dB at the switching frequency

From Notes 5

$$\|G\| = \left(\frac{f}{f_c}\right)^n$$


$$\|G\| = 10^{\left(\frac{-100}{20}\right)} = 1e^{-5}, \quad n = -2 \text{ "40dB/decade"}$$

We want -100dB at $f = 200\text{kHz}$

$$1e^{-5} = \left(\frac{200000}{f_c}\right)^{-2}$$

Solve for required corner f_c

$$f_c \leq 632.45\text{Hz}$$

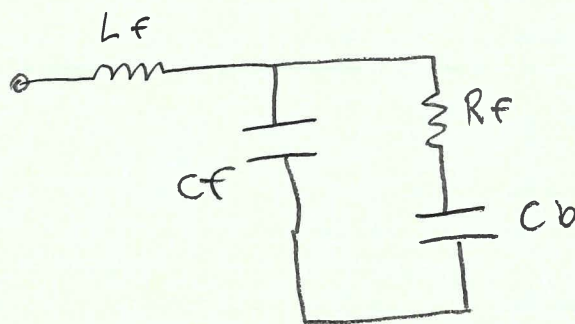

We know $f_c = \frac{1}{2\pi\sqrt{L_f C_f}}$

choose $C_f = 3 \times 47\mu\text{F}$ "AVX Turbo cap"

required $L_f = 449.12\mu\text{H}$

bii) Choose $\|Z_o(j\omega)\|$ to equal the worst case of $\|Z_b(j\omega)\|$ and $\|Z_n(j\omega)\|$
 from the Bode plots, worst case "minimum" impedance occurs at $\|Z_D(j2\pi 1.4e3)\| \approx 14.7 \text{ dB}$

$$14.7 \text{ dB} = 5.43 \Omega$$

set $\|Z_o(j2\pi f_f)\| = (0.3)(5.43) = \|Z_o\|_{\min}$
 \uparrow resonant frequency

$$\|Z_{o\min}\| = 1.6298 \Omega$$

(10.30) from Erickson

$$n = \frac{R_{of}^2}{\|Z_{o\min}\|^2} \left(1 + \sqrt{1 + 4 \frac{\|Z_{o\min}\|^2}{R_{of}^2}} \right)$$

Recall $R_{of} = \sqrt{\frac{L_f}{C_f}}$

$$n \approx 3.6962$$

$$C_b = C_f n$$

$$C_b = 521.17 \mu\text{F} \text{ "electrolytic type"}$$

$$R_f = R_{of} \sqrt{\frac{(2+n)(4+3n)}{2n^2(4+n)}}$$

$$R_f = 1.1410 \Omega$$

