

Johns Hopkins Engineering


# **Power Electronics 525.725**

Module 10 Lecture 10  
Conducted EMI and Filter Design




## 10.1.1 Conducted Electromagnetic Interference (EMI)

Input current  $i_g(t)$  is *pulsating*.

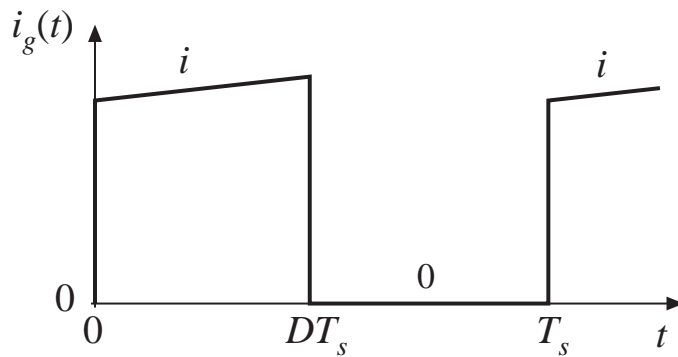

*Buck converter example*

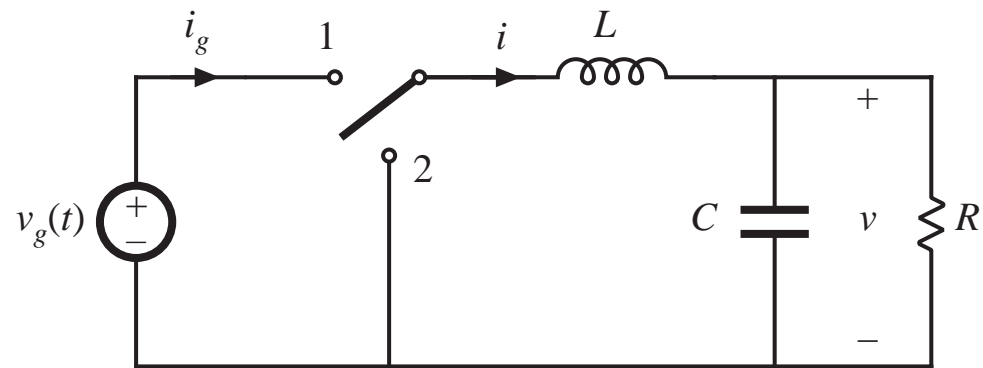


Approximate Fourier series of  $i_g(t)$ :

$$i_g(t) = DI + \sum_{k=1}^{\infty} \frac{2I}{k\pi} \sin(k\pi D) \cos(k\omega t)$$

High frequency current harmonics of substantial amplitude are injected back into  $v_g(t)$  source. These harmonics can interfere with operation of nearby equipment. Regulations limit their amplitude, typically to values of 10  $\mu\text{A}$  to 100  $\mu\text{A}$ .

# Addition of Low-Pass Filter

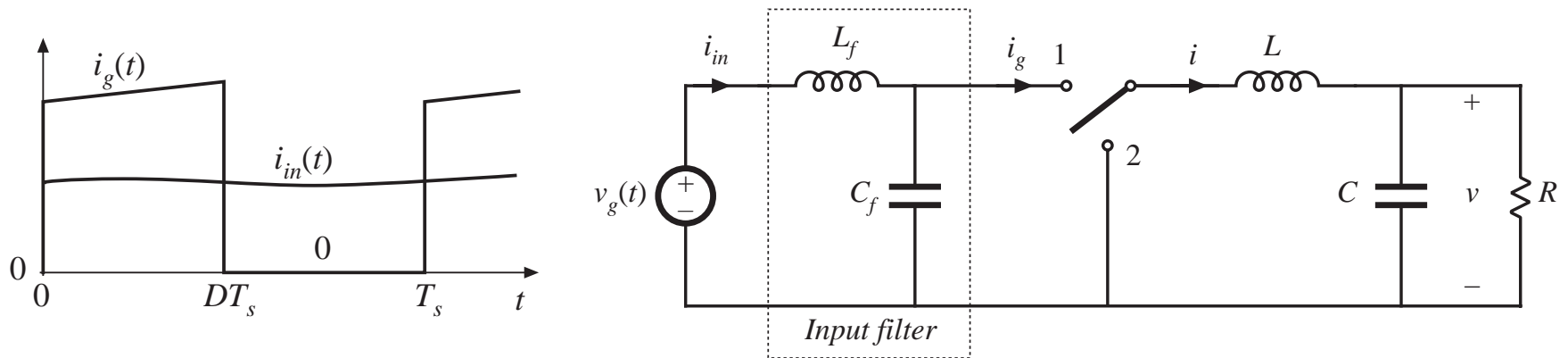

Magnitudes and phases of input current harmonics are modified by input filter transfer function  $H(s)$ :


$$i_{in}(t) = H(0)DI + \sum_{k=1}^{\infty} \|H(kj\omega)\| \frac{2I}{k\pi} \sin(k\pi D) \cos(k\omega t + \angle H(kj\omega))$$

The input filter may be required to attenuate the current harmonics by factors of 80 dB or more.

## 10.1.2 The Input Filter Design Problem

A typical design approach:

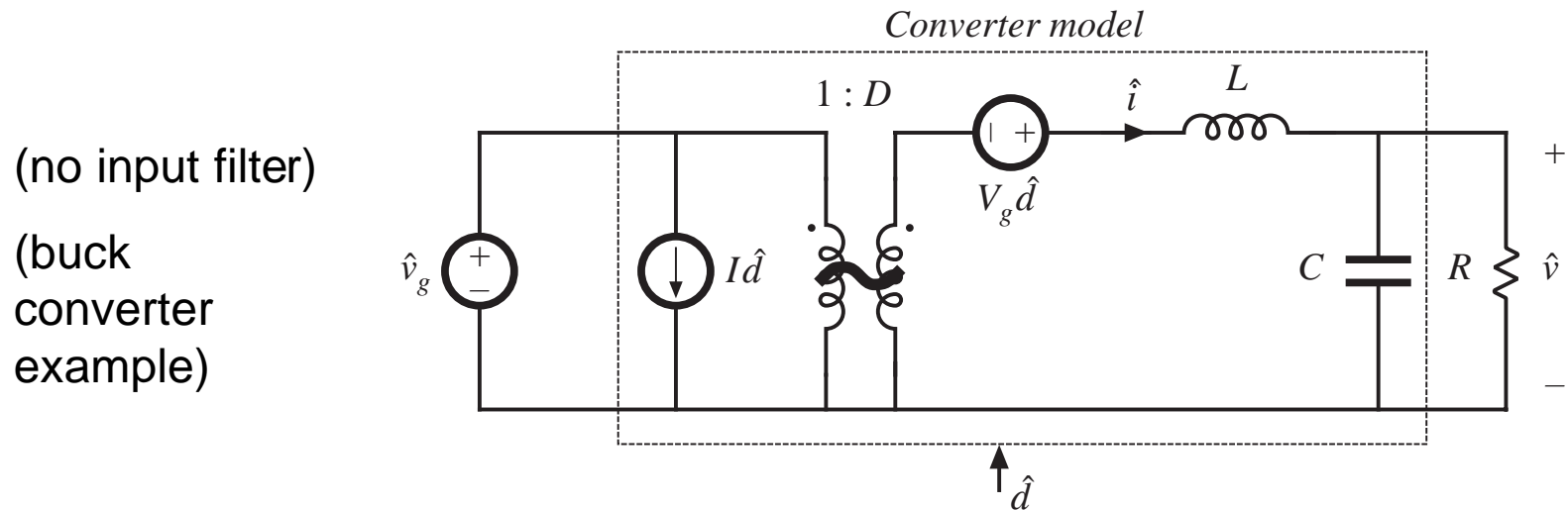
1. Engineer designs switching regulator that meets specifications (stability, transient response, output impedance, etc.). In performing this design, a basic converter model is employed, such as the one below:




## Input Filter Design Problem, p. 2

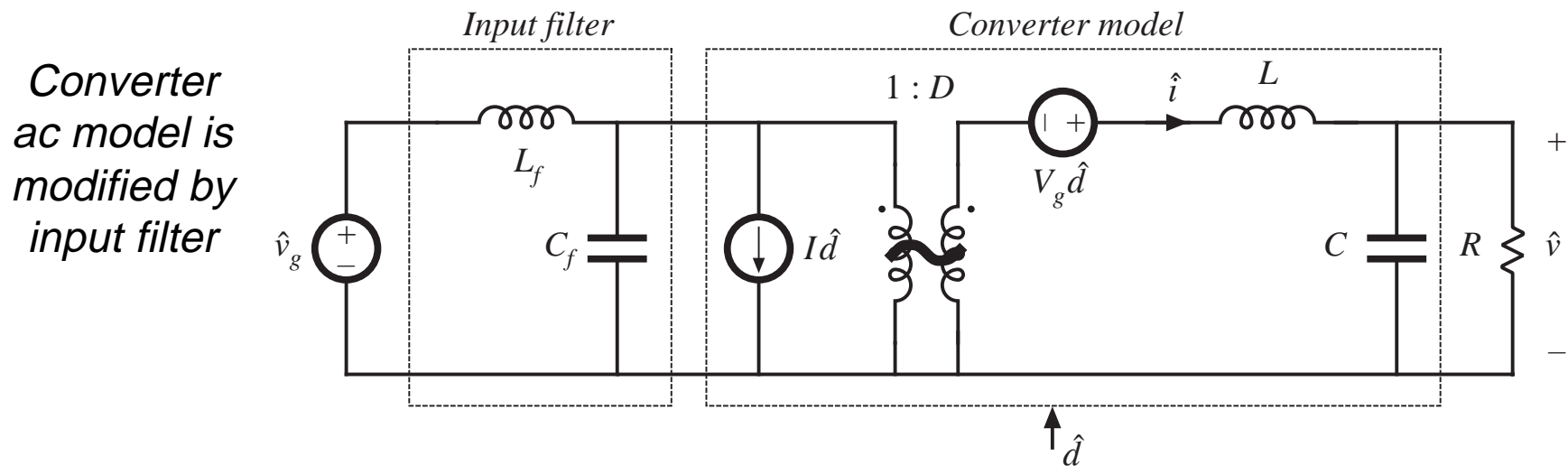2. Later, the problem of conducted EMI is addressed. An input filter is added, that attenuates harmonics sufficiently to meet regulations.
3. A new problem arises: the controller no longer meets dynamic response specifications. The controller may even become unstable.

Reason: input filter changes converter transfer functions



## Input Filter Design Problem, p. 3

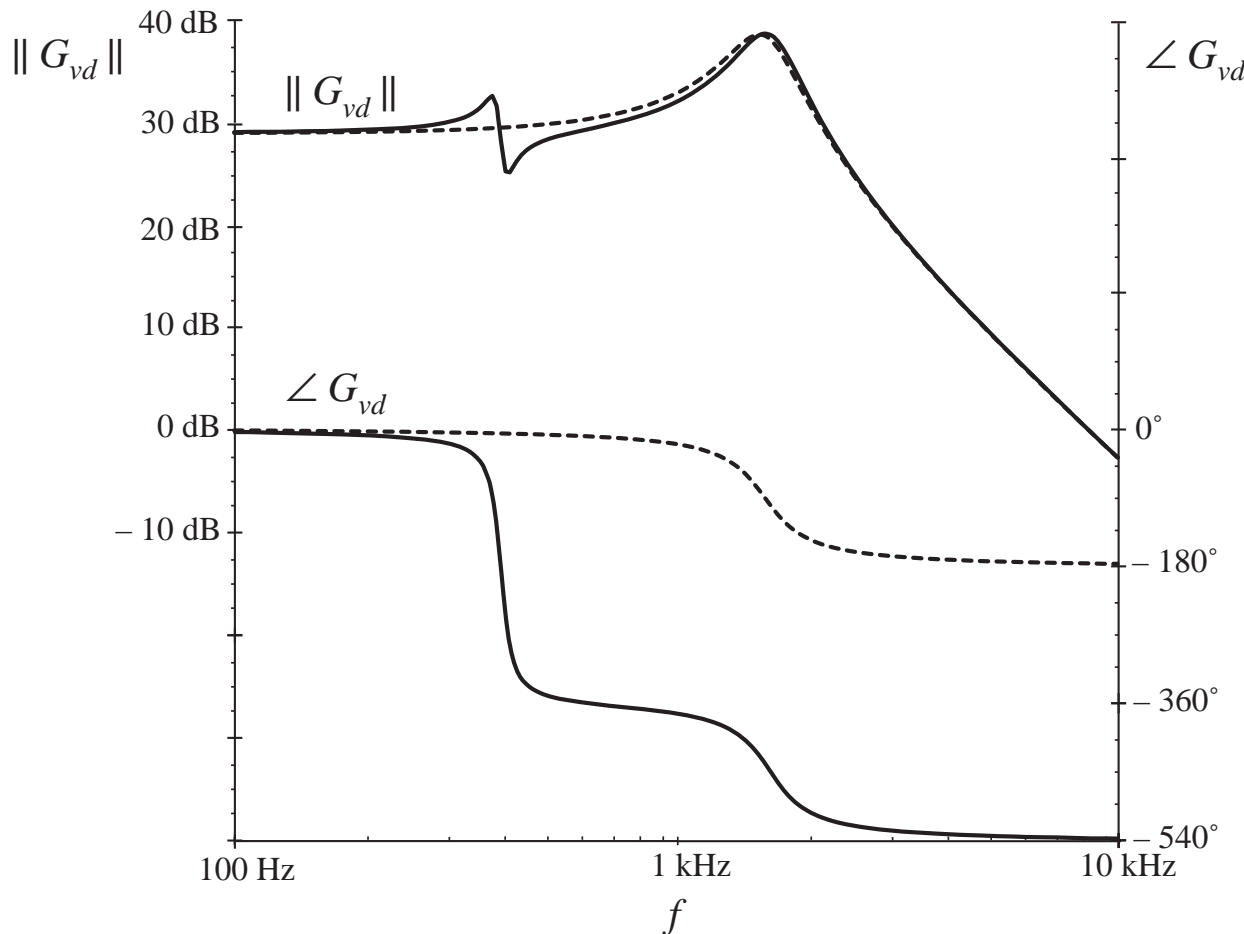


Effect of  $L$ - $C$  input filter on control-to-output transfer function  $G_{vd}(s)$ , buck converter example.

*Dashed lines:* original magnitude and phase

*Solid lines:* with addition of input filter
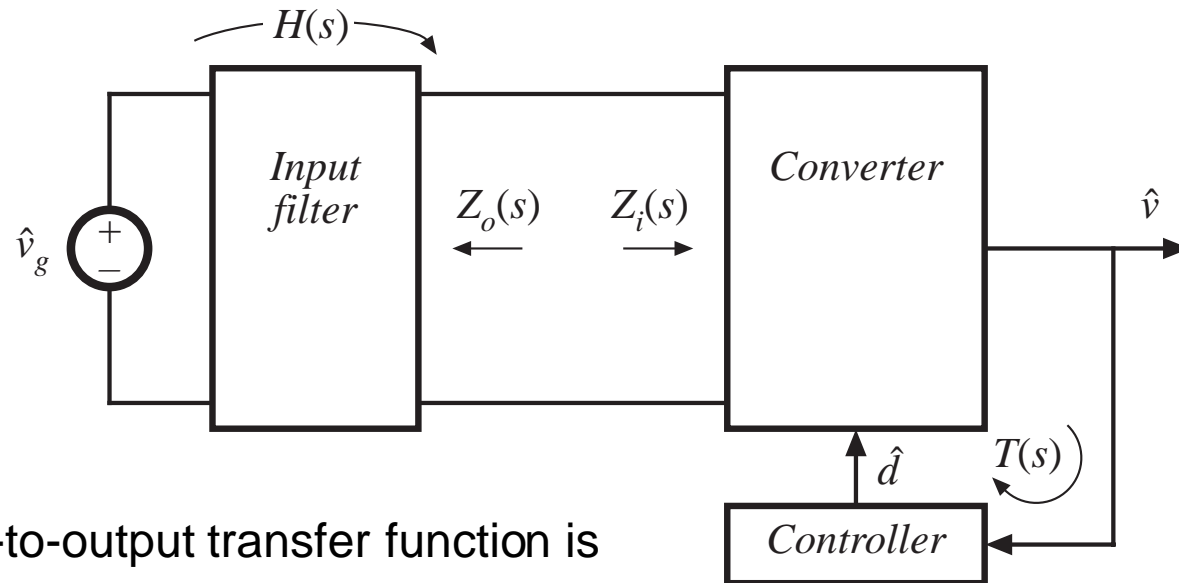
## 10.2 Effect of an Input Filter on Converter Transfer Functions



Control-to-output transfer function is


$$G_{vd}(s) = \left. \frac{\hat{v}(s)}{\hat{d}(s)} \right|_{\hat{v}_g(s)=0}$$

# Determination of $G_{vd}(s)$

$$G_{vd}(s) = \left. \frac{\hat{v}(s)}{\hat{d}(s)} \right|_{\hat{v}_g(s)=0}$$

$\hat{v}_g(s)$  source  $\rightarrow$  short circuit

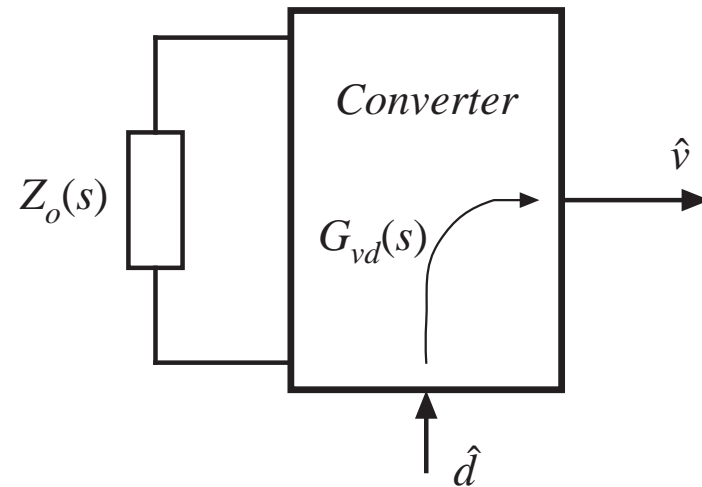$Z_o(s)$  = output impedance of  
input filter



We will use Middlebrook's Extra Element Theorem to show that the input filter modifies  $G_{vd}(s)$  as follows:

$$G_{vd}(s) = \left( G_{vd}(s) \Big|_{Z_o(s)=0} \right) \frac{\left( 1 + \frac{Z_o(s)}{Z_N(s)} \right)}{\left( 1 + \frac{Z_o(s)}{Z_D(s)} \right)}$$



## 10.2.2 Impedance Inequalities

---

$$G_{vd}(s) = \left( G_{vd}(s) \Big|_{Z_o(s)=0} \right) \frac{\left( 1 + \frac{Z_o(s)}{Z_N(s)} \right)}{\left( 1 + \frac{Z_o(s)}{Z_D(s)} \right)}$$

The *correction factor*  $\frac{\left( 1 + \frac{Z_o(s)}{Z_N(s)} \right)}{\left( 1 + \frac{Z_o(s)}{Z_D(s)} \right)}$  shows how the input filter modifies the transfer function  $G_{vd}(s)$ .

The correction factor has a magnitude of approximately unity provided that the following inequalities are satisfied:

$$\begin{aligned} \|Z_o\| &\ll \|Z_N\|, \text{ and} \\ \|Z_o\| &\ll \|Z_D\| \end{aligned}$$

These provide design criteria, which are relatively easy to apply.

# How an input filter changes $G_{vd}(s)$

## Summary of result

---

$$G_{vd}(s) = \left( G_{vd}(s) \Big|_{Z_o(s)=0} \right) \frac{\left( 1 + \frac{Z_o(s)}{Z_N(s)} \right)}{\left( 1 + \frac{Z_o(s)}{Z_D(s)} \right)}$$


$G_{vd}(s) \Big|_{Z_o(s)=0}$  is the original transfer function, before addition of input filter

$Z_D(s) = Z_i(s) \Big|_{\hat{d}(s)=0}$  is the converter input impedance, with  $\hat{d}$  set to zero

$Z_N(s) = Z_i(s) \Big|_{\hat{v}(s) \xrightarrow{\text{null}} 0}$  is the converter input impedance, with the output  $\hat{v}$  nulled to zero

(see Appendix C for proof using EET)

## 10.2.1 Discussion

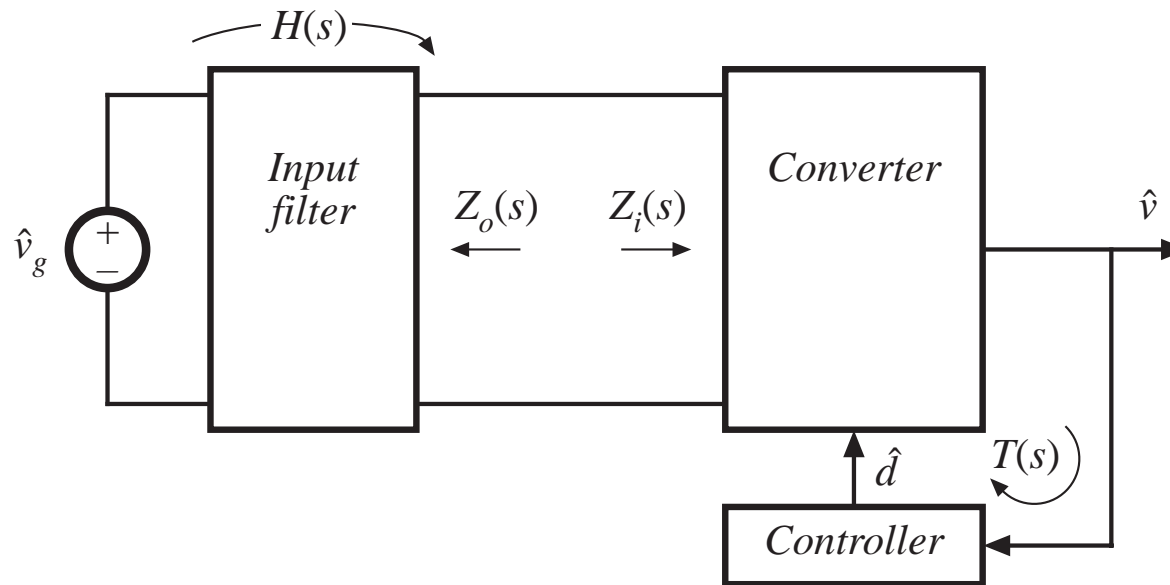

$Z_N(s) = Z_i(s) \Big|_{\hat{v}(s) \xrightarrow{\text{null}} 0}$  is the converter input impedance, with the output  $\hat{v}$  nulled to zero

Note that this is the same as the function performed by an ideal controller, which varies the duty cycle as necessary to maintain zero error of the output voltage. So  $Z_N$  coincides with the input impedance when an ideal feedback loop perfectly regulates the output voltage.

# Design criteria for basic converters


**Table 10.1** Input filter design criteria for basic converters

Converter	$Z_N(s)$	$Z_D(s)$	$Z_e(s)$
Buck	$-\frac{R}{D^2}$	$\frac{R}{D^2} \frac{\left(1 + s\frac{L}{R} + s^2LC\right)}{(1 + sRC)}$	$\frac{sL}{D^2}$
Boost	$-D'^2R \left(1 - \frac{sL}{D'^2R}\right)$	$D'^2R \frac{\left(1 + s\frac{L}{D'^2R} + s^2\frac{LC}{D'^2}\right)}{(1 + sRC)}$	$sL$
Buck–boost	$-\frac{D'^2R}{D^2} \left(1 - \frac{sDL}{D'^2R}\right)$	$\frac{D'^2R}{D^2} \frac{\left(1 + s\frac{L}{D'^2R} + s^2\frac{LC}{D'^2}\right)}{(1 + sRC)}$	$\frac{sL}{D^2}$


# 10.3 Buck Converter Example

## 10.3.1 Effect of undamped input filter

*Buck converter with input filter*


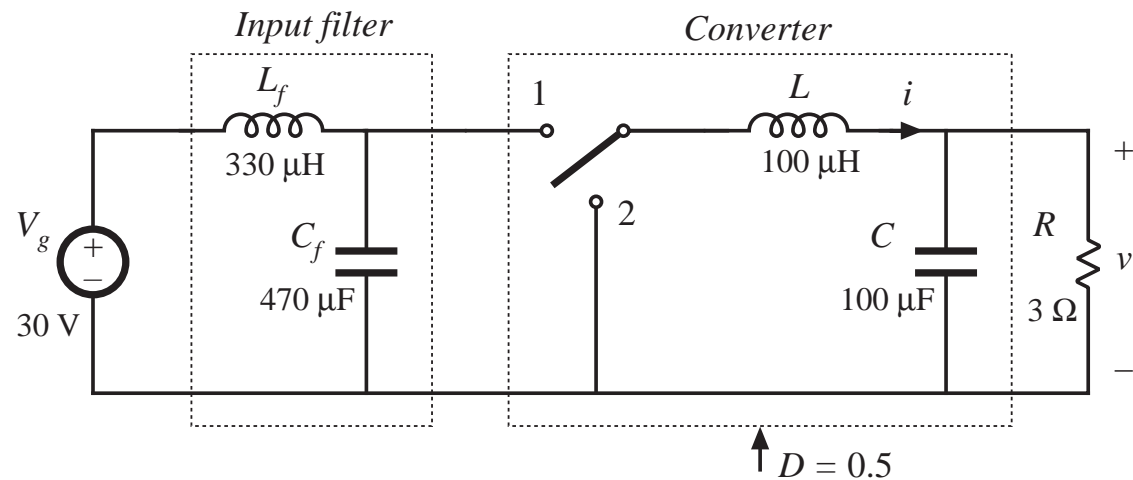


*Small-signal model*

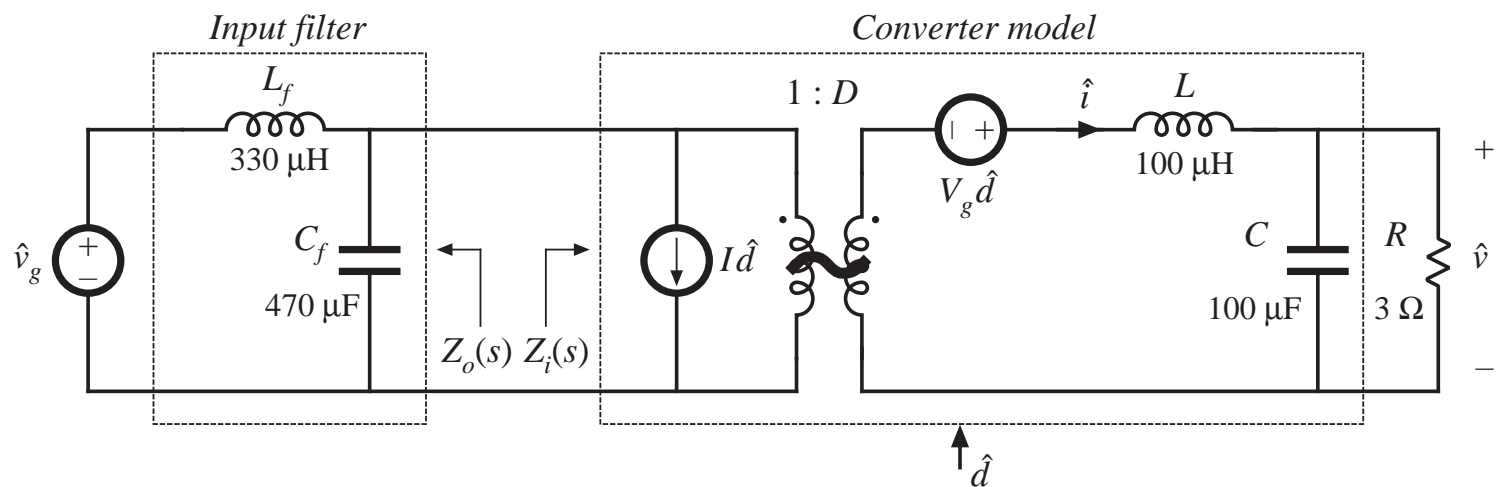

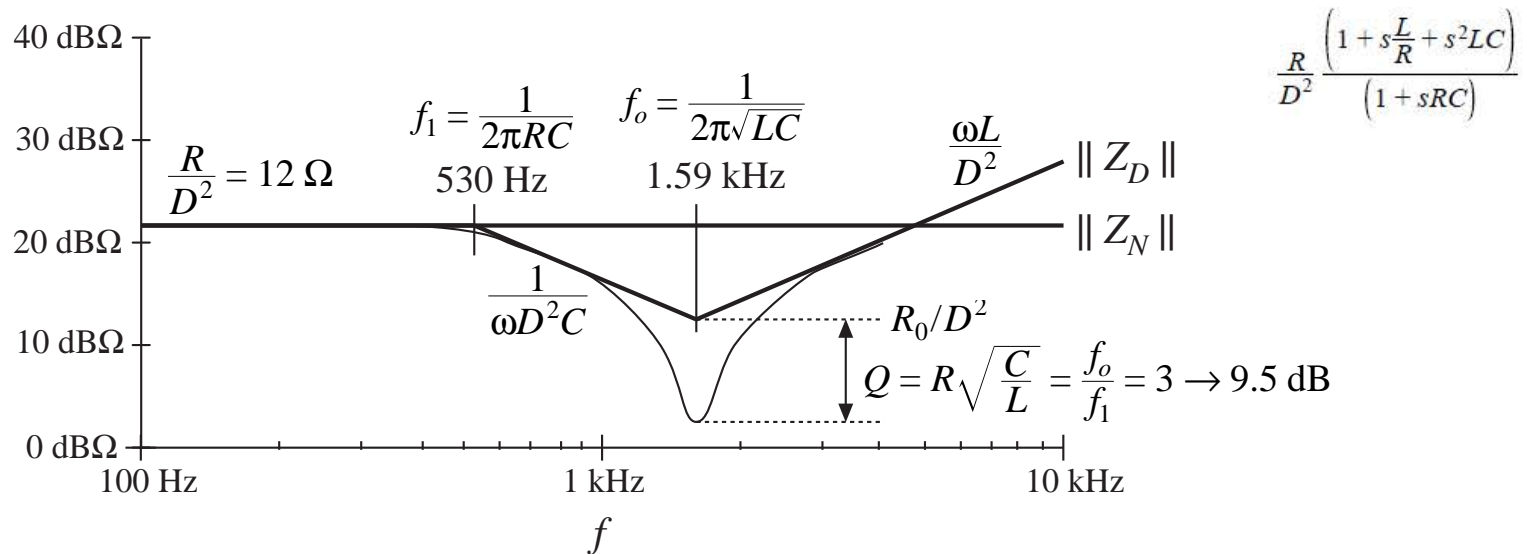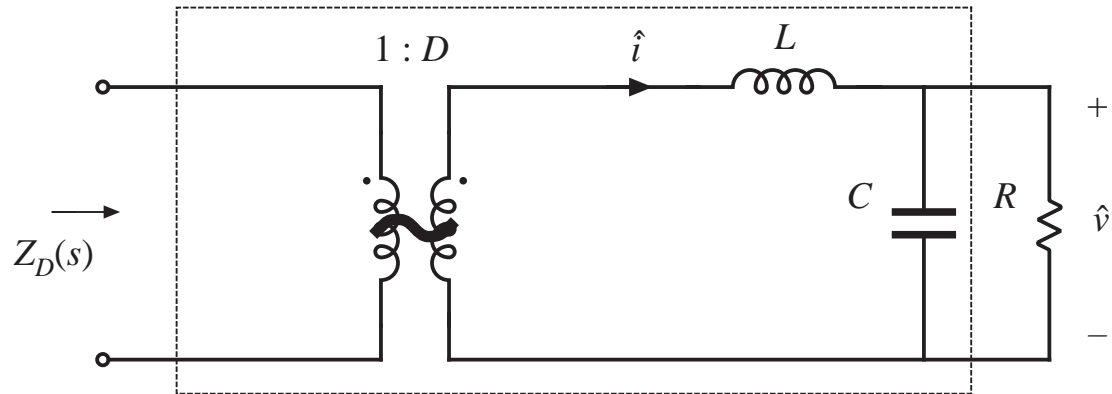
# Determination of $Z_D$

$$Z_D(s) = \frac{1}{D^2} \left( sL + R \parallel \frac{1}{sC} \right)$$



# Determination of $Z_N$

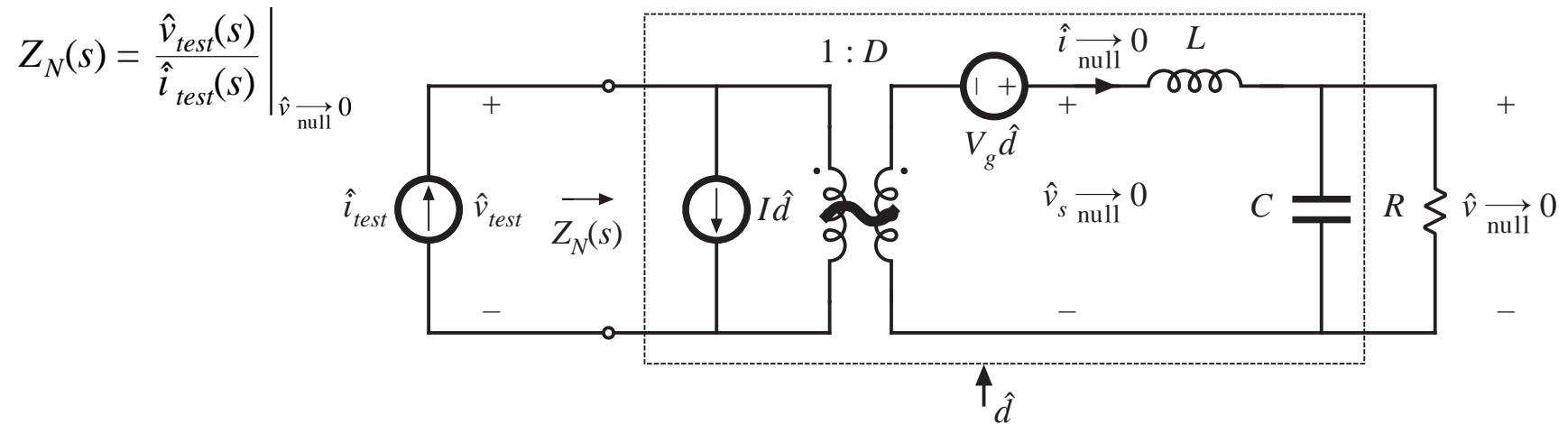

Solution:


$$\hat{i}_{test}(s) = I\hat{d}(s)$$

$$\hat{v}_{test}(s) = -\frac{V_g\hat{d}(s)}{D}$$


Hence,

$$Z_N(s) = \frac{\left(-\frac{V_g\hat{d}(s)}{D}\right)}{(I\hat{d}(s))} = -\frac{R}{D^2}$$

# $Z_o$ of undamped input filter

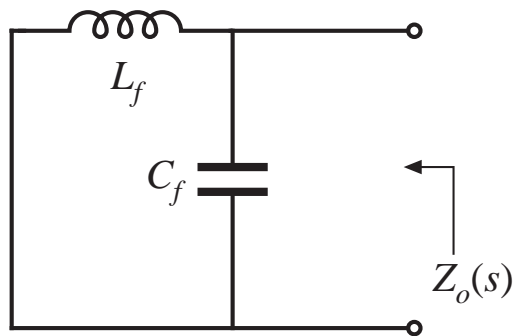
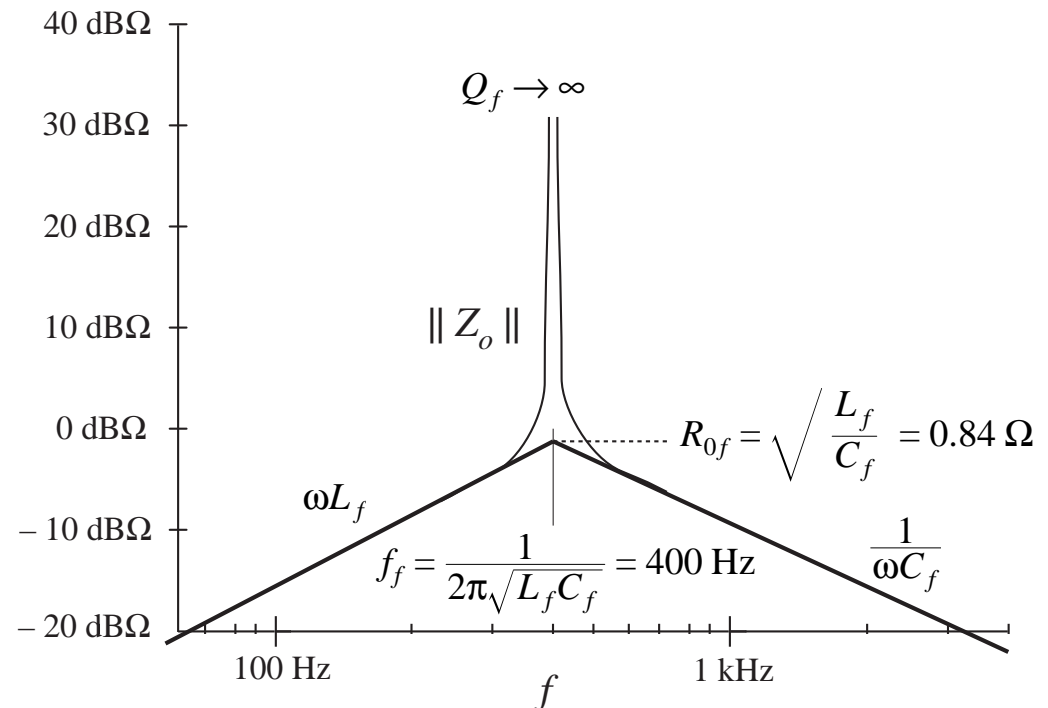
$$Z_o(s) = sL_f \parallel \frac{1}{sC_f}$$





No resistance, hence poles are undamped (infinite  $Q$ -factor).

In practice, losses limit  $Q$ -factor; nonetheless,  $Q_f$  may be very large.


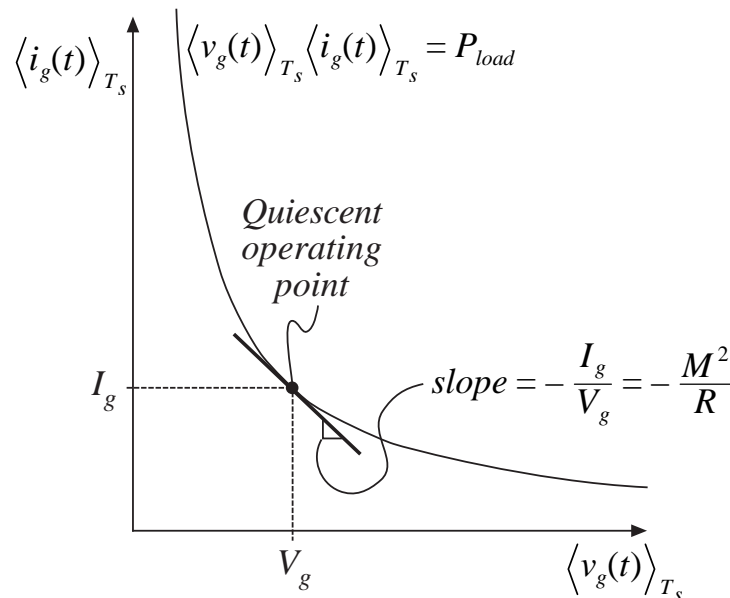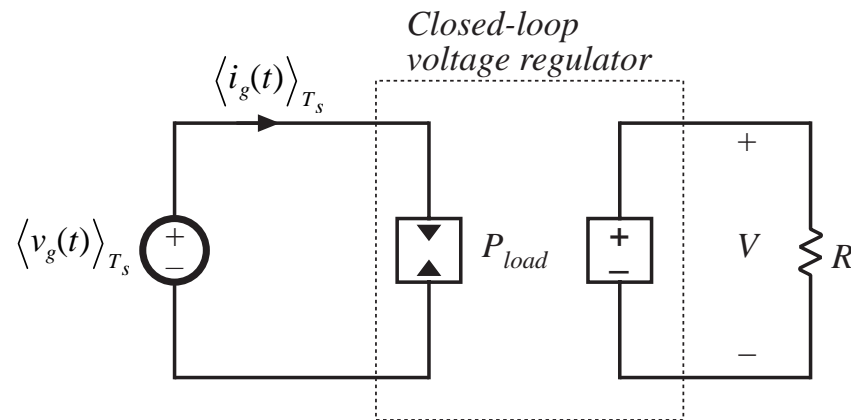
# When the output voltage is perfectly regulated



- For a given load characteristic, the output power  $P_{load}$  is independent of the converter input voltage
- If losses are negligible, then the input port  $i$ - $v$  characteristic is a power sink characteristic, equal to  $P_{load}$ :

$$\langle v_g(t) \rangle_{T_s} \langle i_g(t) \rangle_{T_s} = P_{load}$$

- Incremental input resistance is negative, and is equal to:

$$-\frac{R}{M^2}$$

(same as dc asymptote of  $Z_N$ )

# Negative resistance oscillator

---

It can be shown that the closed-loop converter input impedance is given by:

$$\frac{1}{Z_i(s)} = \frac{1}{Z_N(s)} \frac{T(s)}{1 + T(s)} + \frac{1}{Z_D(s)} \frac{1}{1 + T(s)}$$

where  $T(s)$  is the converter loop gain.


At frequencies below the loop crossover frequency, the input impedance is approximately equal to  $Z_N$ , which is a negative resistance.

When an undamped or lightly damped input filter is connected to the regulator input port, the input filter can interact with  $Z_N$  to form a *negative resistance oscillator*.

Design criteria

$$\|Z_o\| \ll \|Z_N\|, \text{ and}$$


$$\|Z_o\| \ll \|Z_D\|$$

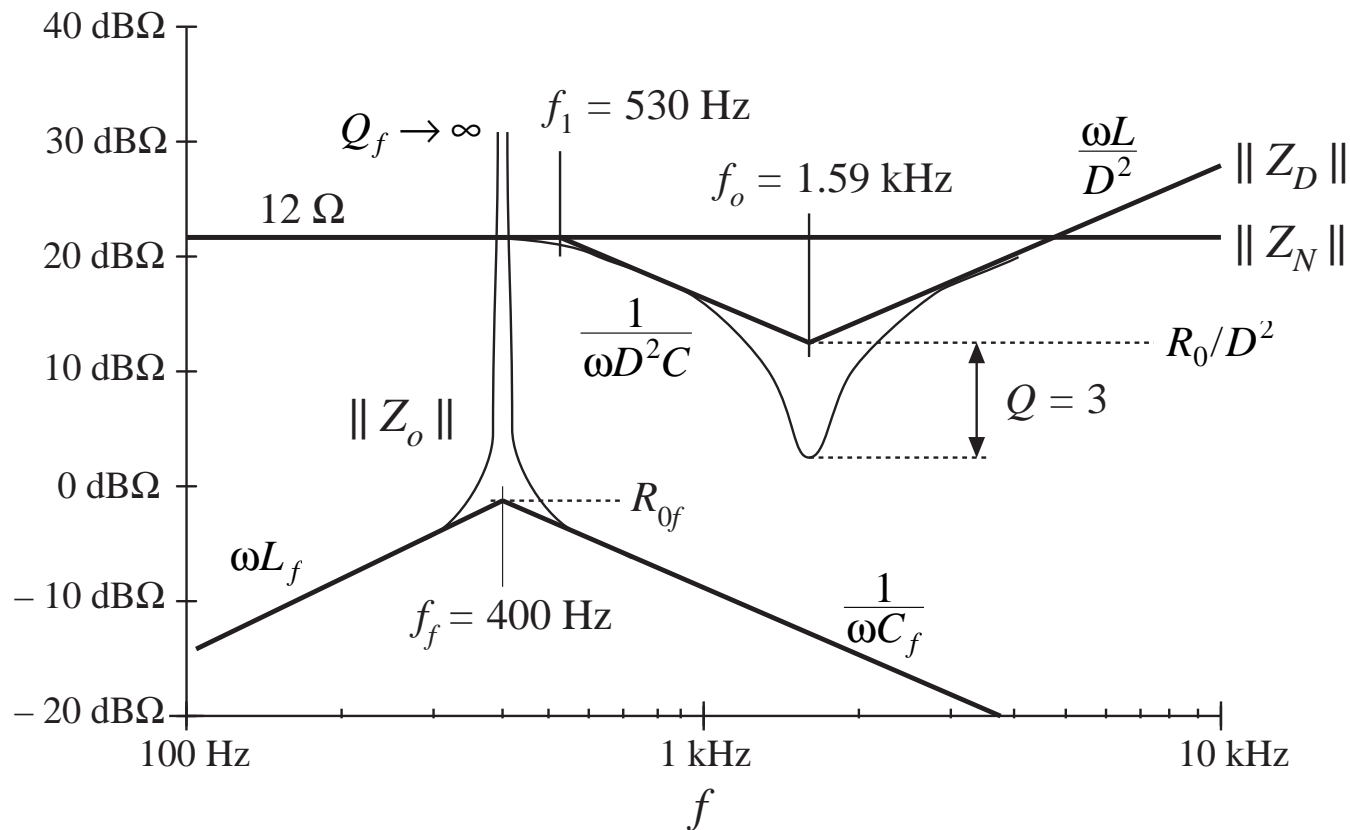


Can meet inequalities everywhere except at resonant frequency  $f_f$

Need to damp input filter!

# Resulting correction factor

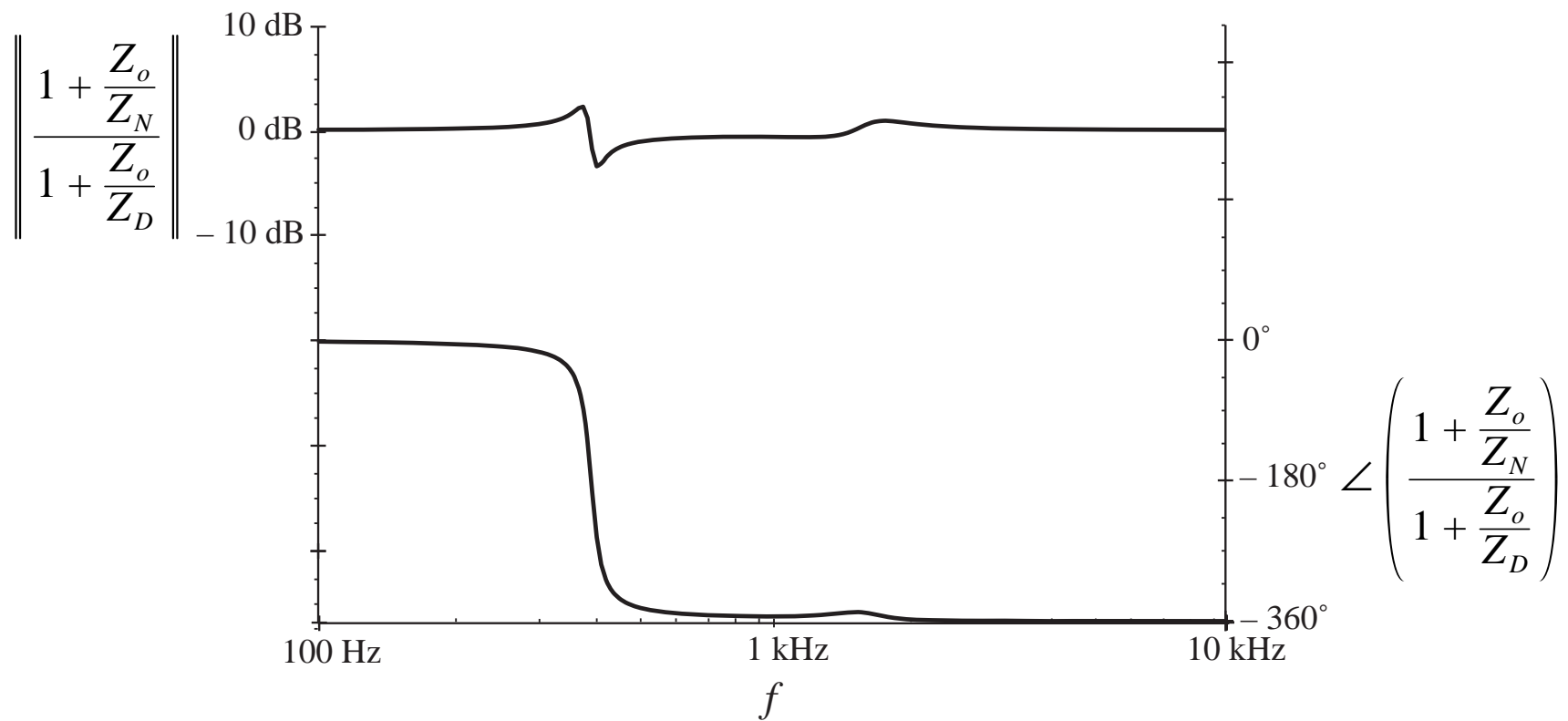


# Resulting transfer function


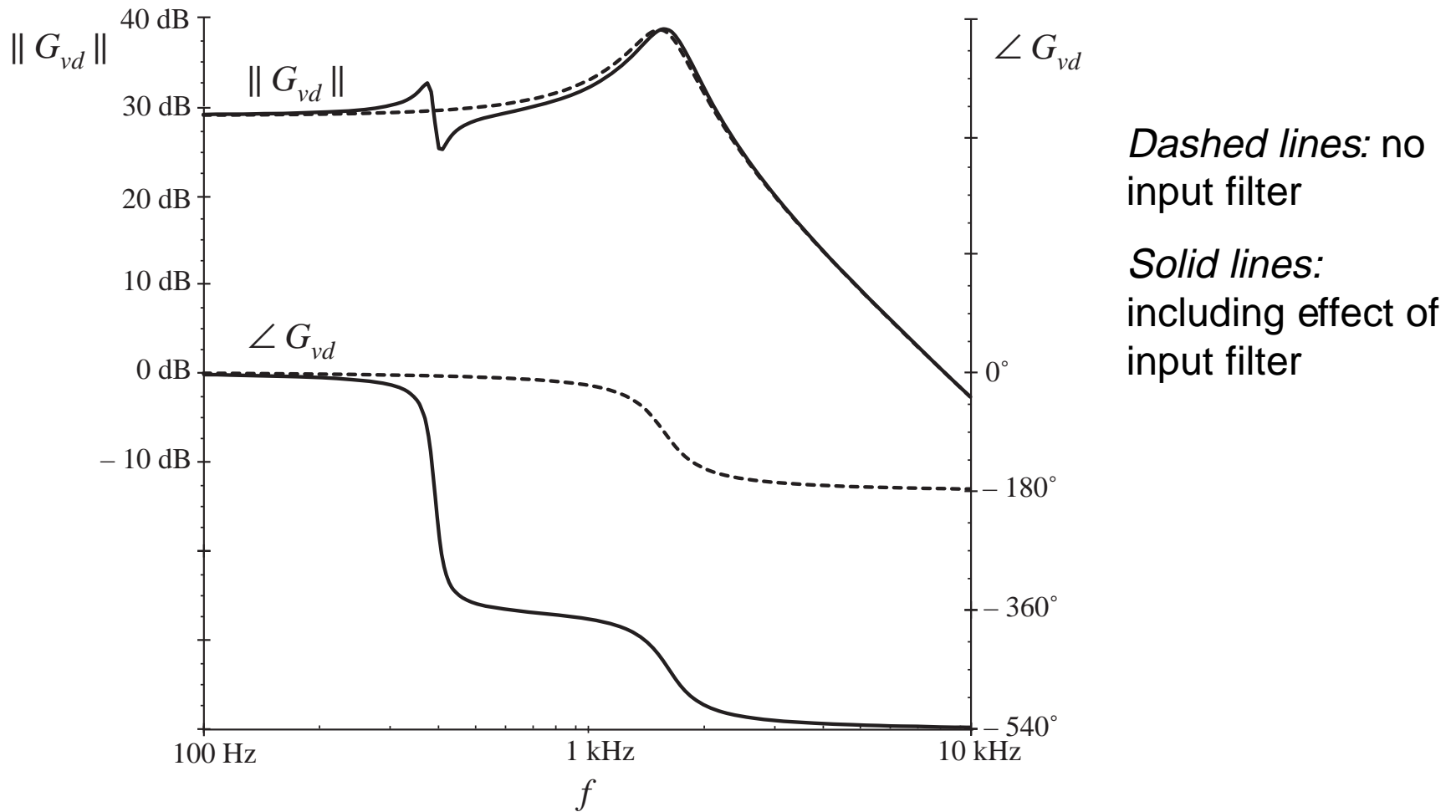


## 10.3.2 Damping the input filter

Undamped filter:

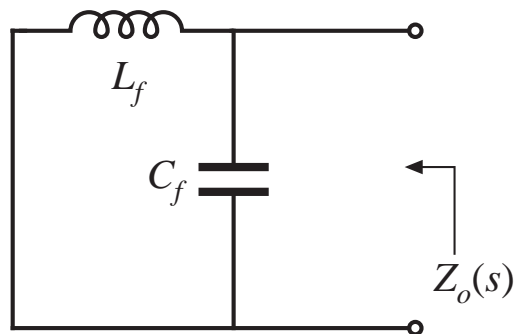

Two possible approaches:

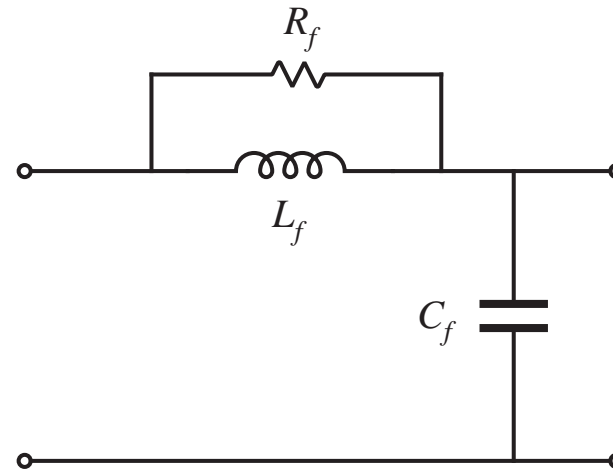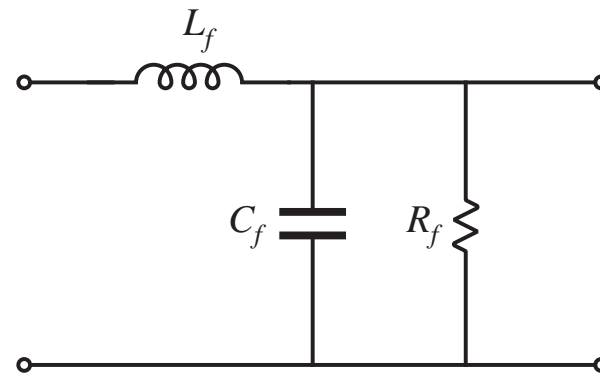

## Addition of $R_f$ across $C_f$



To meet the requirement  $R_f \ll \|Z_N\|$ :

$$R_f \ll \frac{R}{D^2}$$


The power loss in  $R_f$  is  $V_g^2 / R_f$ ,  
which is larger than the load power!

A solution: add dc blocking  
capacitor  $C_b$ .

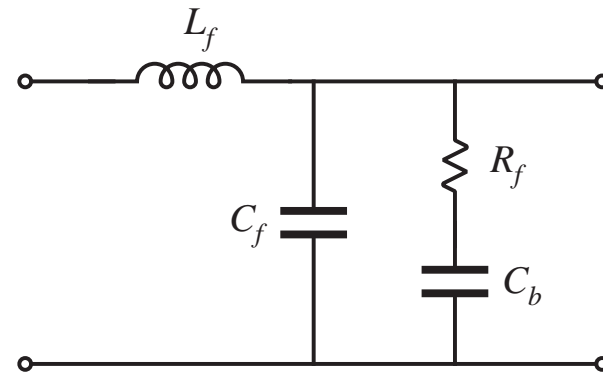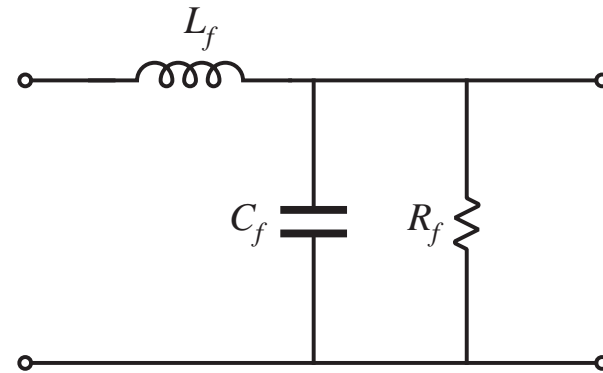
Choose  $C_b$  so that its impedance is  
sufficiently smaller than  $R_f$  at the  
filter resonant frequency.



# Damped input filter

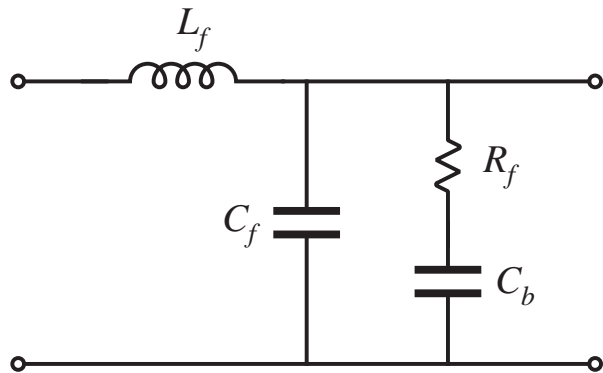


$\|Z_o\|$ , with large  $C_b$

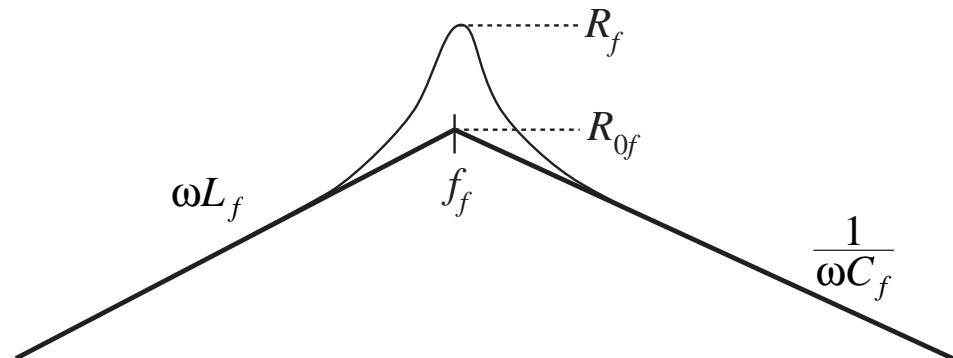



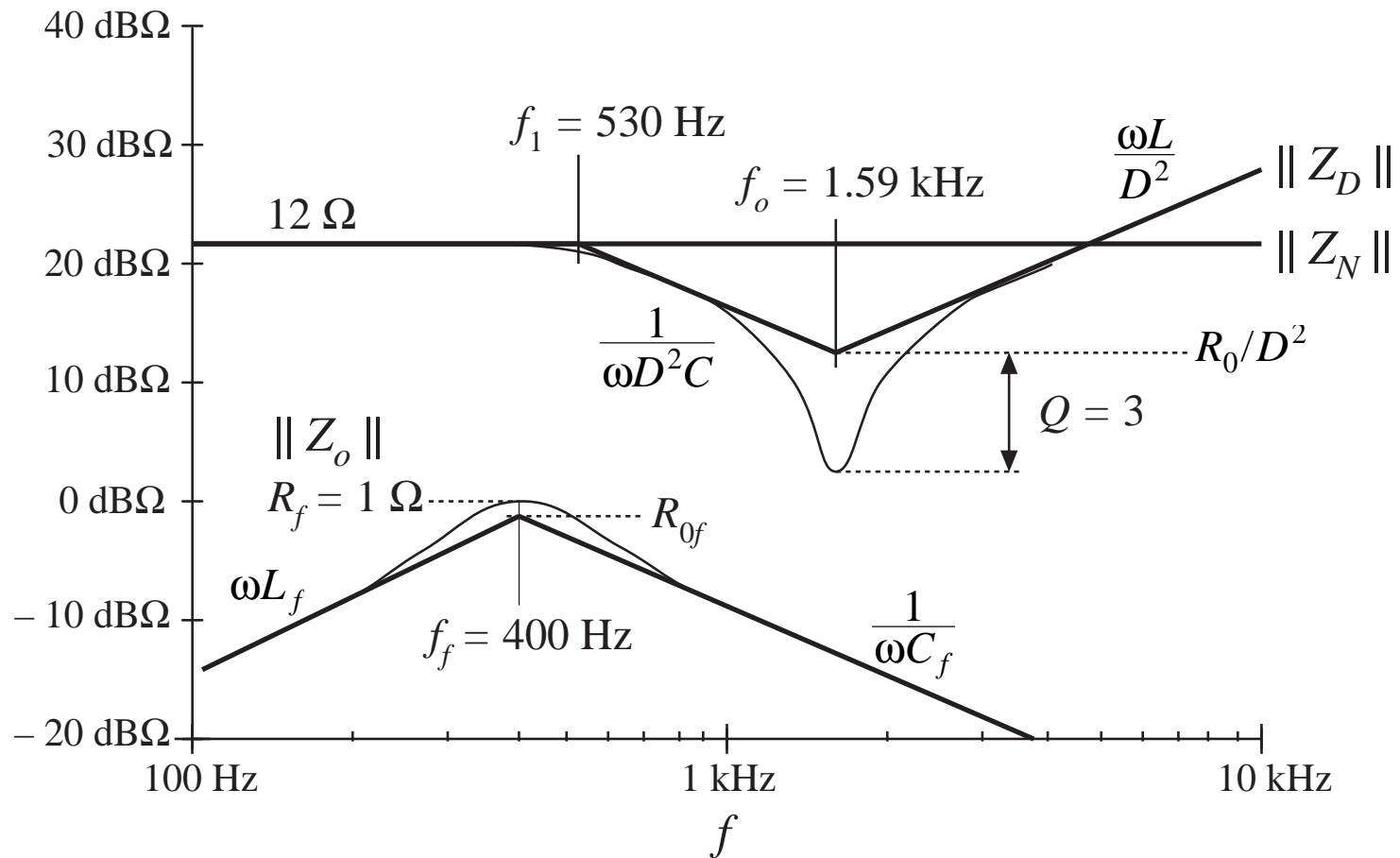
# Design criteria, with damped input filter




# Resulting transfer function

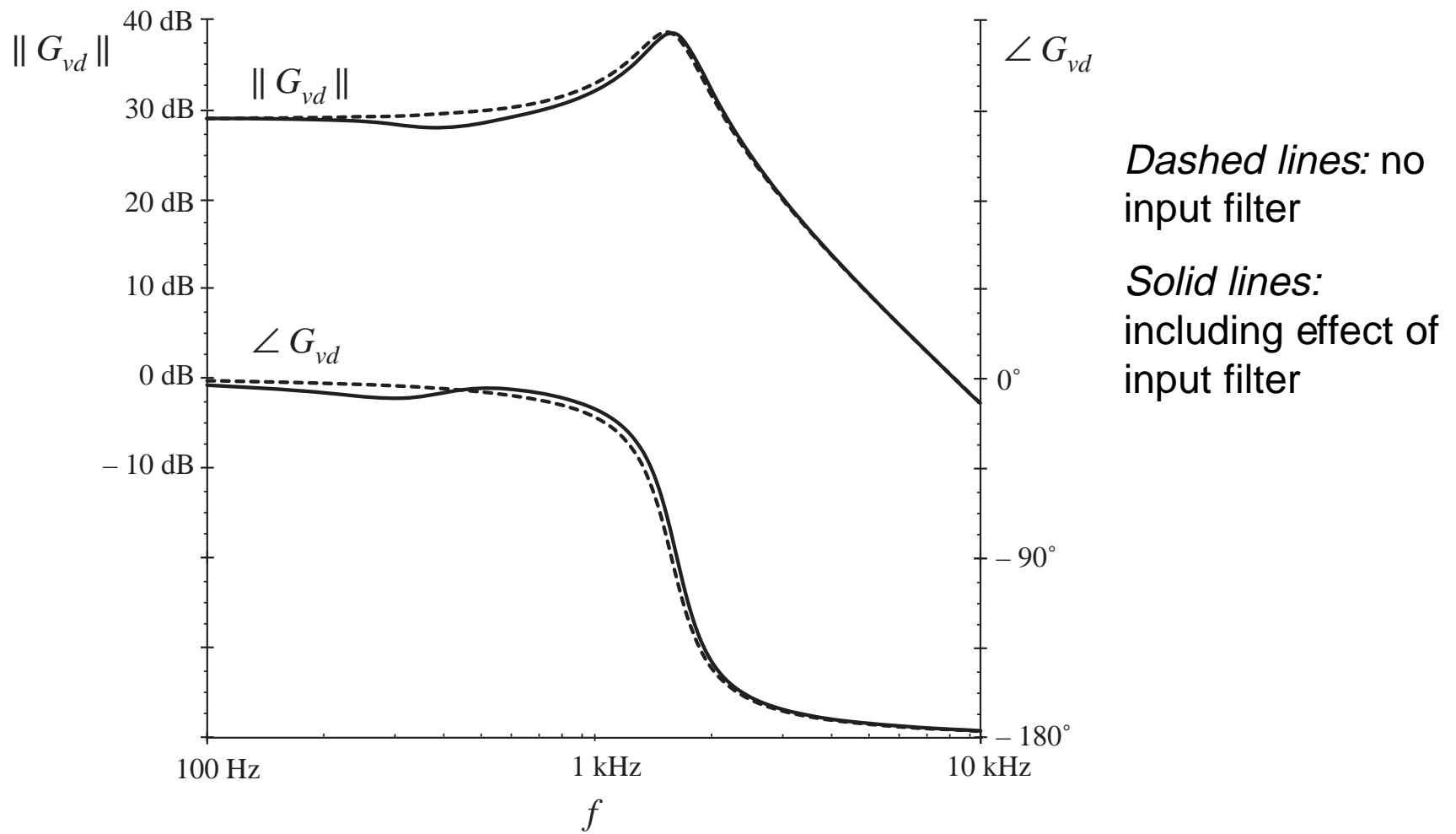


## 10.4 Design of a Damped Input Filter


$R_f$ - $C_b$  Parallel Damping

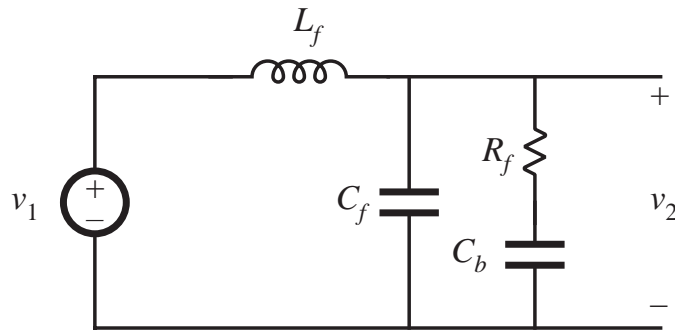

$R_f$ - $L_b$  Series Damping

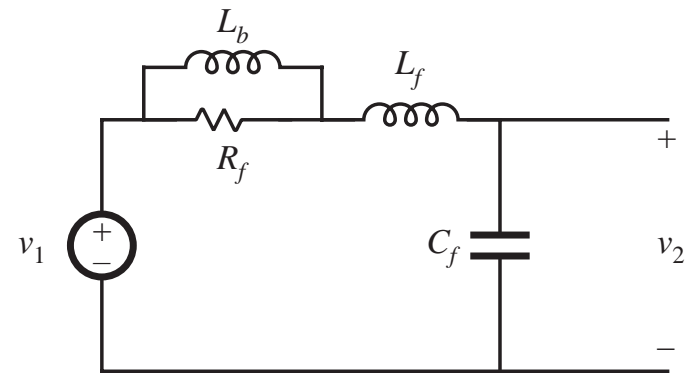


$R_f$ - $L_b$  Parallel Damping

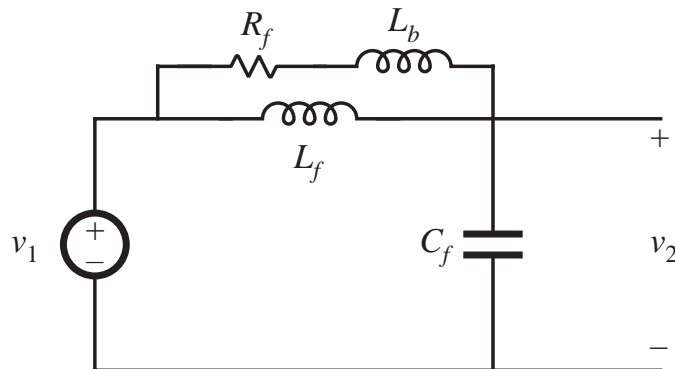

- Size of  $C_b$  or  $L_b$  can become very large
- Need to optimize design


# Dependence of $\|Z_o\|$ on $R_f$

## $R_f$ - $L_b$ Parallel Damping

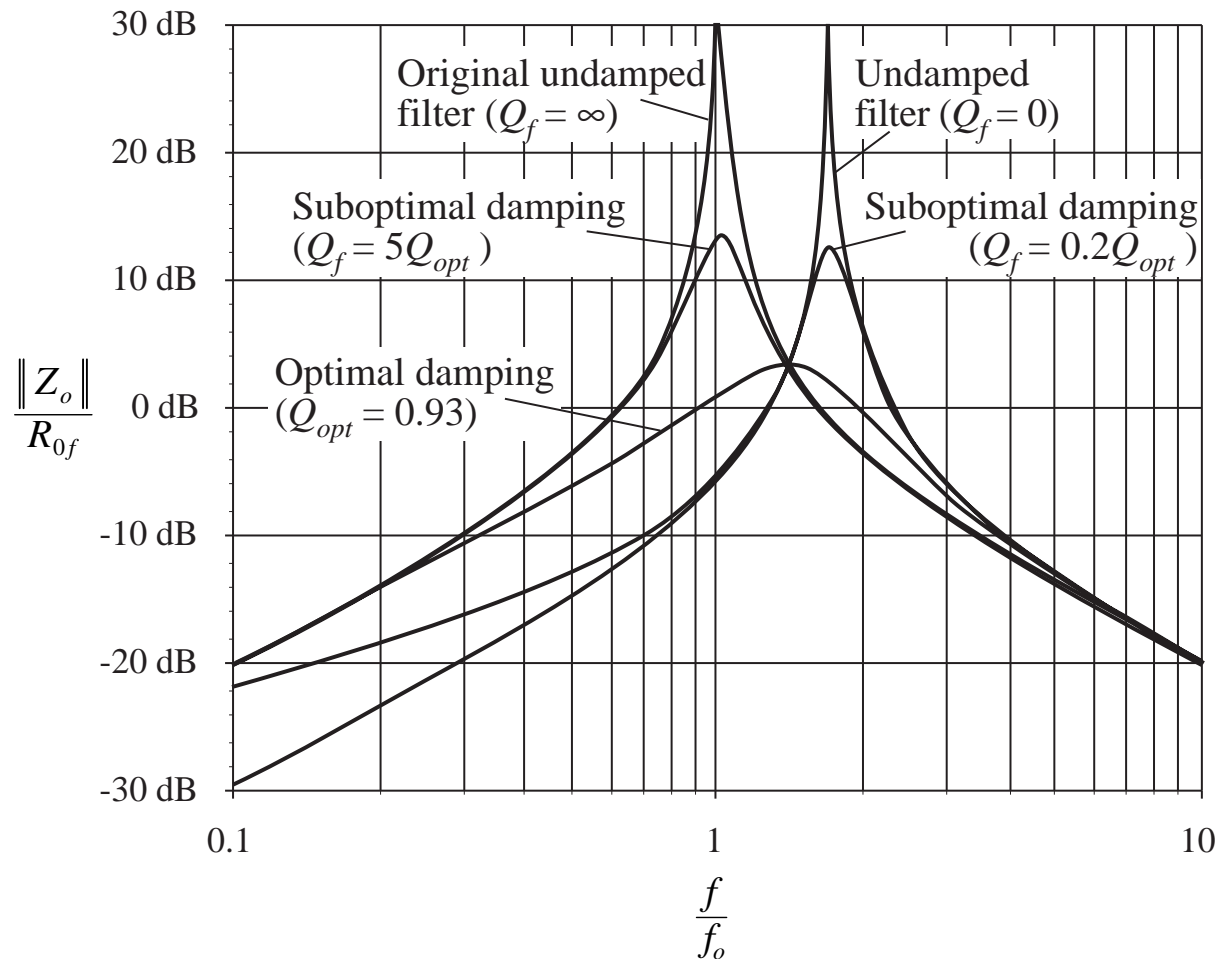

For this example,  
 $n = L_b/L = 0.516$

## 10.4.1 $R_f$ - $C_b$ Parallel Damping

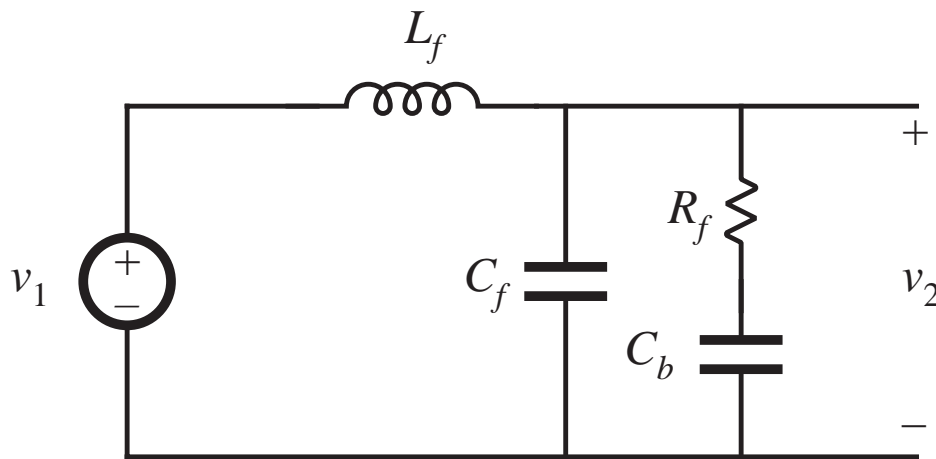

- Filter is damped by  $R_f$
- $C_b$  blocks dc current from flowing through  $R_f$
- $C_b$  can be large in value, and is an element to be optimized

# Optimal design equations

## $R_f$ – $C_b$ Parallel Damping

---

Define  $n = \frac{C_b}{C_f}$

The value of the peak output impedance for the optimum design is

$$\|Z_o\|_{\text{mm}} = R_{0f} \frac{\sqrt{2(2+n)}}{n} \quad \text{where } R_{0f} = \text{characteristic impedance of original undamped input filter}$$

Given a desired value of the peak output impedance, can solve above equation for  $n$ . The required value of damping resistance  $R_f$  can then be found from:

$$Q_{\text{opt}} = \frac{R_f}{R_{0f}} = \sqrt{\frac{(2+n)(4+3n)}{2n^2(4+n)}}$$

The peak occurs at the frequency

$$f_m = f_f \sqrt{\frac{2}{2+n}}$$


# Example

## Buck converter of Section 10.3.2


$$n = \frac{R_{0f}^2}{\|Z_o\|_{\text{mm}}^2} \left( 1 + \sqrt{1 + 4 \frac{\|Z_o\|_{\text{mm}}^2}{R_{0f}^2}} \right) = 2.5 \quad R_f = R_{0f} \sqrt{\frac{(2+n)(4+3n)}{2n^2(4+n)}} = 0.67 \, \Omega$$
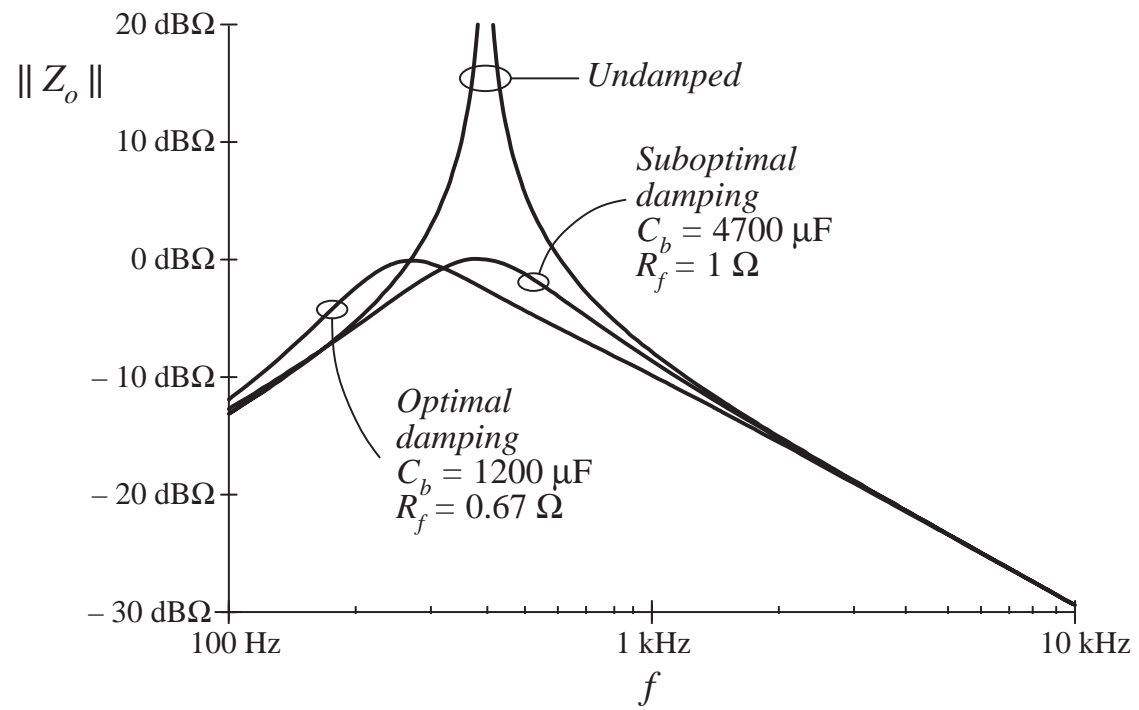
### Comparison of designs

Optimal damping achieves same peak output impedance, with much smaller  $C_b$ .


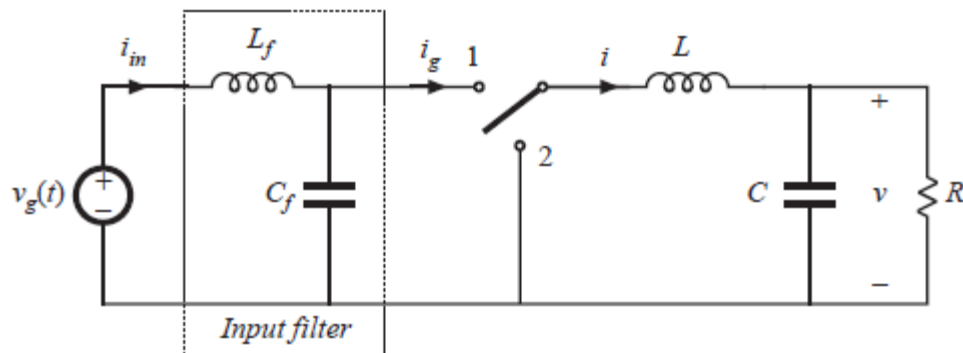
# SIMULINK SIMULATION BUCK CONVERTER INPUT FILTER STUDY



$$V_g = 28 \text{ V}$$

$$V = 12 \text{ V}$$

$$P_{\text{out}} = 100 \text{ W}$$

$$f_{\text{sw}} = 100 \text{ kHz}$$

$$L_{\text{out}} = 79.602 \text{ uH}$$


$$C_{\text{out}} = 5.2083 \text{ uF}$$




# There are two mfiles and 1 simulink file

- dft\_code\_importingsimulink.m
  - This file pulls in a variable from work space to perform DFT
- buck\_switching\_filter.m
  - This is your file to set up the simulation
- buck\_wfilter\_switching
  - Simulink file

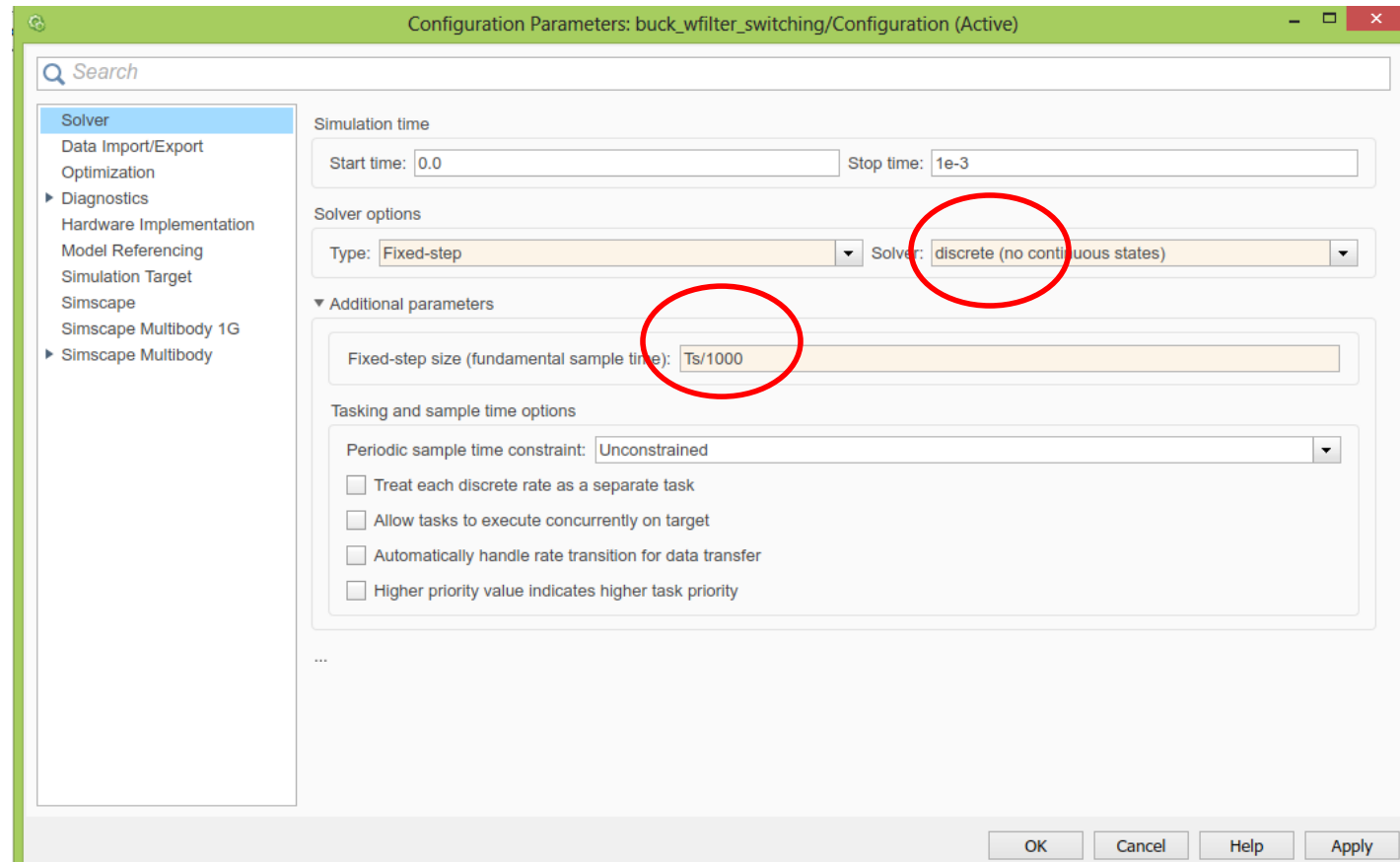
# Run without Filter - Setup to run fixed time step ( $T_s/1000$ )


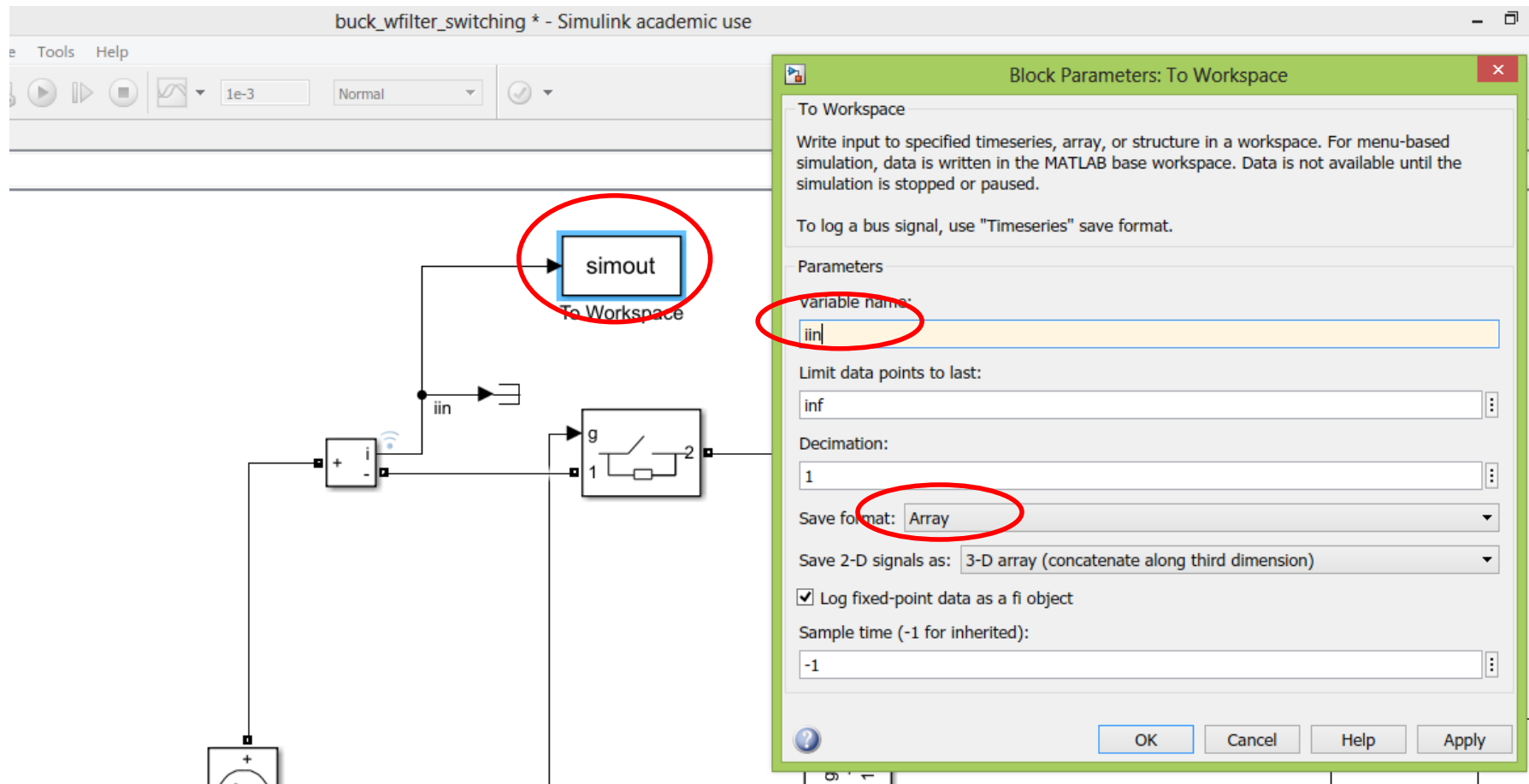
# Output input current to workspace – add simout block – name variable “iin”



# Fill in mfile inputs for DFT run

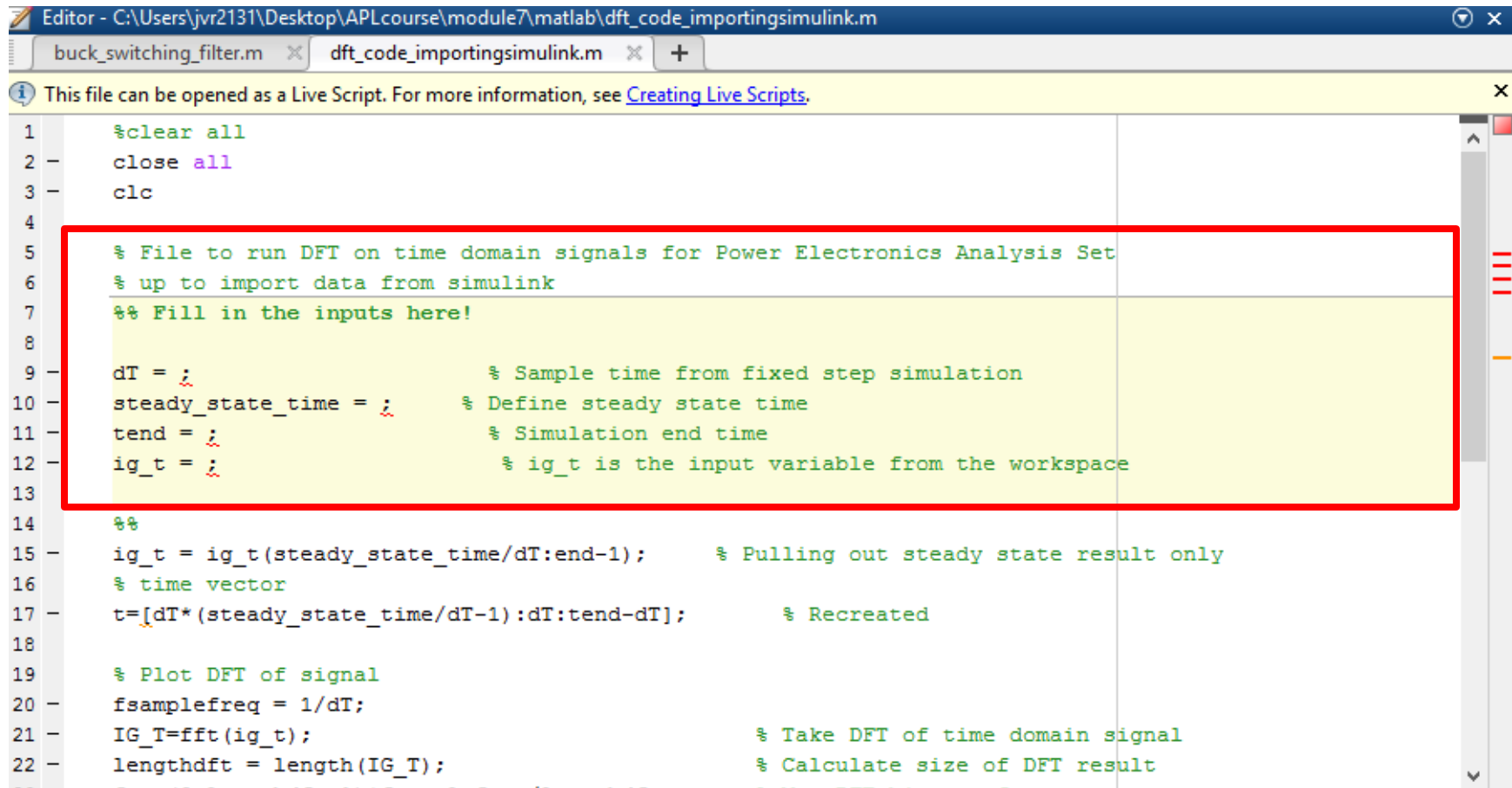

The image shows a MATLAB Editor window with the following content:

```
Editor - C:\Users\jvr2131\Desktop\APLcourse\module7\matlab\dft_code_importingsimulink.m
buck_switching_filter.m x dft_code_importingsimulink.m x +
This file can be opened as a Live Script. For more information, see Creating Live Scripts.
1 %clear all
2 close all
3 clc
4
5 % File to run DFT on time domain signals for Power Electronics Analysis Set
6 % up to import data from simulink
7 %% Fill in the inputs here!
8
9 dT = ; % Sample time from fixed step simulation
10 steady_state_time = ; % Define steady state time
11 tend = ; % Simulation end time
12 ig_t = ; % ig_t is the input variable from the workspace
13
14 %%
15 ig_t = ig_t(steady_state_time/dT:end-1); % Pulling out steady state result only
16 % time vector
17 t=[dT*(steady_state_time/dT-1):dT:tend-dT]; % Recreated
18
19 % Plot DFT of signal
20 fsamplefreq = 1/dT;
21 IG_T=fft(ig_t); % Take DFT of time domain signal
22 lengthdft = length(IG_T); % Calculate size of DFT result
```

A red rectangular box highlights the section of code from line 5 to line 13, which contains the instructions for filling in the input variables for the DFT run.

# Run file – Confirm steady state

